

# ANALOG CIRCUITS DESIGN

---


AE4: Operational Amplifiers III,  
Stability

# Course overview

1. Basic concepts:
  - The condition for oscillation
  - The phase margin concept
2. 1<sup>st</sup> order circuits
3. 2<sup>nd</sup> order circuits
  - Optimal phase margin
  - Unity-gain stable OPA
4. Higher order circuits
  - overview
  - Practical examples 1: The inverting/non-inverting amplifier
  - Practical examples 2: The voltage follower
5. Oscillators
  - What for?
  - Relaxation oscillators
  - Harmonic quartz crystal oscillators
6. Appendix A
7. Appendix B
8. Appendix C
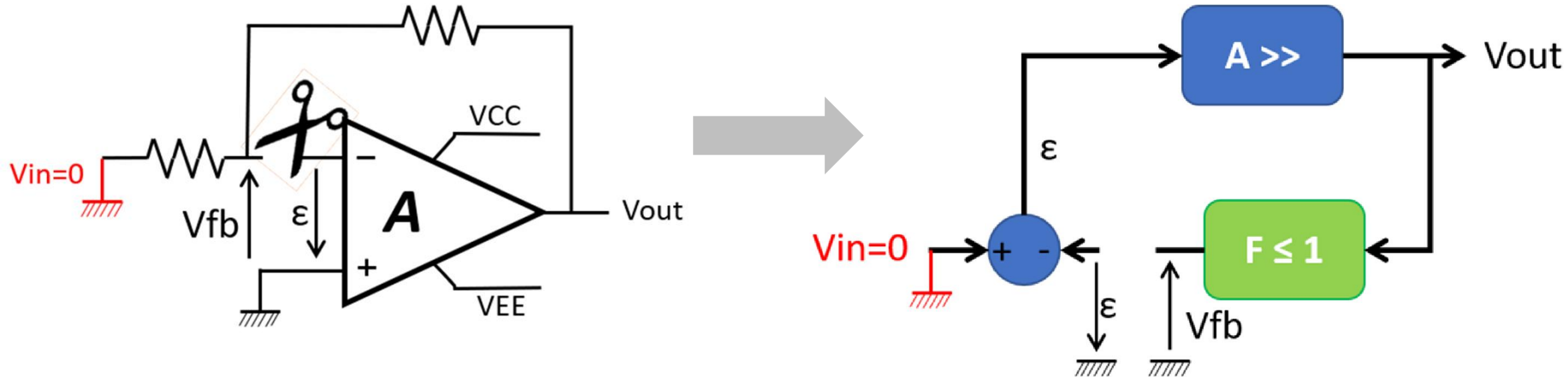
## 1. Basic concepts: The condition for oscillation

- Stability is evaluated in open loop, without signal



- Loop gain:  $\frac{V_{fb}}{\varepsilon} = AF$

$|AF| > 1$  and  $\varphi_{AF} \ll 180^\circ \rightarrow$  stable (negative feedback)


$|AF| = 1$  and  $\varphi_{AF} = 180^\circ \rightarrow$  harmonic oscillator (Barkhausen criterion)

$|AF| \ll 1$  and  $\varphi_{AF} > 180^\circ \rightarrow$  stable

## 1. Basic concepts: The phase margin concept

➤ Stability is ensured if  $\varphi_{AF}$  is « sufficiently far away » from  $180^\circ$  when  $|AF| = 1$

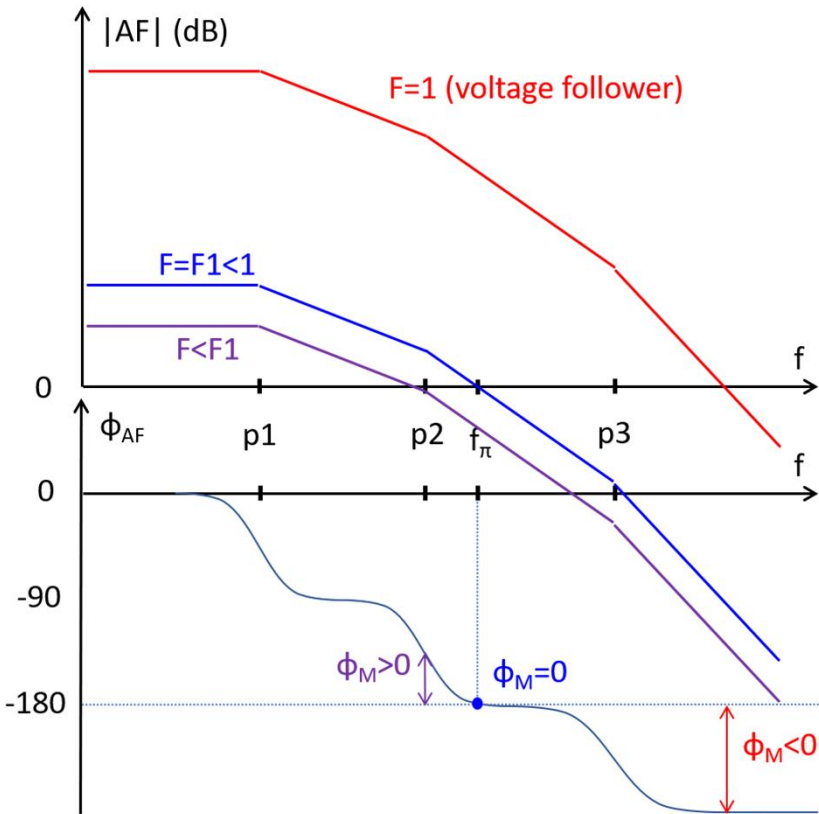➤ Phase margin  $\varphi_M$ : difference between circuit phase  $\varphi_{AF}$  and  $180^\circ$



Example: 3-pole circuit with different values of feedback factor  $F$

- $F=1$  (worst case): phase margin is negative → UNSTABLE
  - $F=F_1$ : phase margin is zero, gain is 0dB → OSCILLATOR @  $f=f_\pi$
  - $F < F_1$ : phase margin is positive, → STABLE
- A maximum value for  $F$  (i.e. a minimum closed-loop gain) exists to ensure stability



➤ How much phase margin is necessary?

## 2. 1<sup>st</sup> order circuits

➤ When a pole ( $p_1$ ) is really dominant (other poles occur when gain is less than one)

➤ Open-loop gain:  $A(s)F \approx \frac{A_0 F}{1 + \frac{s}{p_1}}$

( $A_0$ : value of A when  $f=0$ )

➤ One single pole  $\rightarrow \varphi_{AF} \leq 90^\circ$   
UNCONDITIONALLY STABLE

➤ Closed-loop gain:  $H(s) \approx \frac{A_0}{(1 + A_0 F) \left(1 + \frac{s}{(1 + A_0 F)p_1}\right)} = \frac{H_0}{1 + \frac{s}{p'_1}}$

➤ Gain-Bandwidth product (GBW) is constant:

$$GBW = H_0 p'_1 = \frac{A_0}{(1 + A_0 F)} (1 + A_0 F) p_1 = A_0 p_1 = cte$$

### 3. 2<sup>nd</sup> order circuits

➤ When two poles ( $p_1, p_2$ ) exist,  $p_1$  is not really dominant


➤ Open-loop gain:  $A(s)F \approx \frac{A_0 F}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)}$

➤ Two poles  $\rightarrow \varphi_{AF}$  reaches  $-180^\circ$  when  $f = \infty \rightarrow$  MATHEMATICALLY STABLE but....

➤ Closed-loop gain ( $\omega_p=1\text{rd/s}$ )\*:


$$H(s) = \frac{H_0}{s^2 + s\frac{1}{Q} + 1}$$

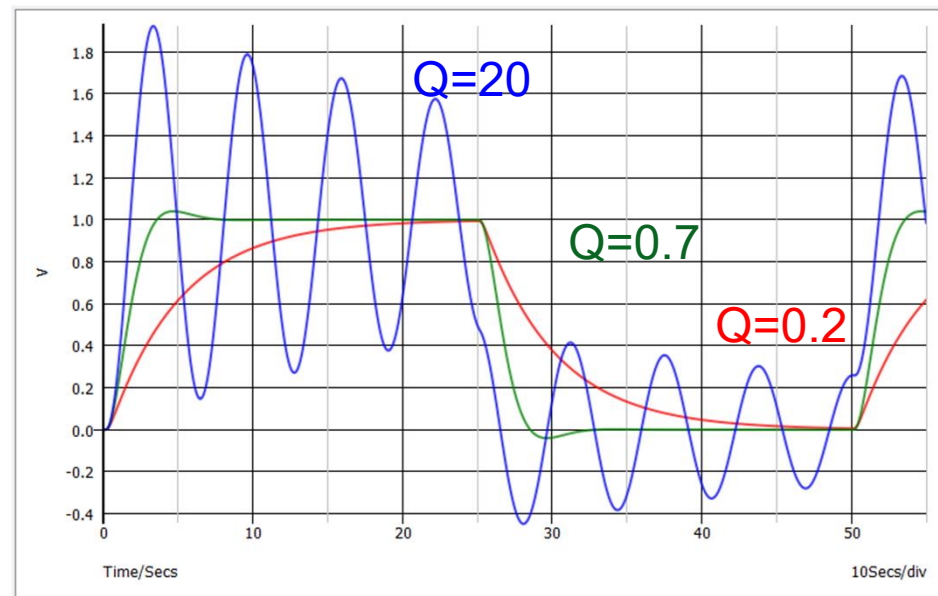Time response may exhibit unacceptable overshoots or oscillations



\*: see details in appendix A
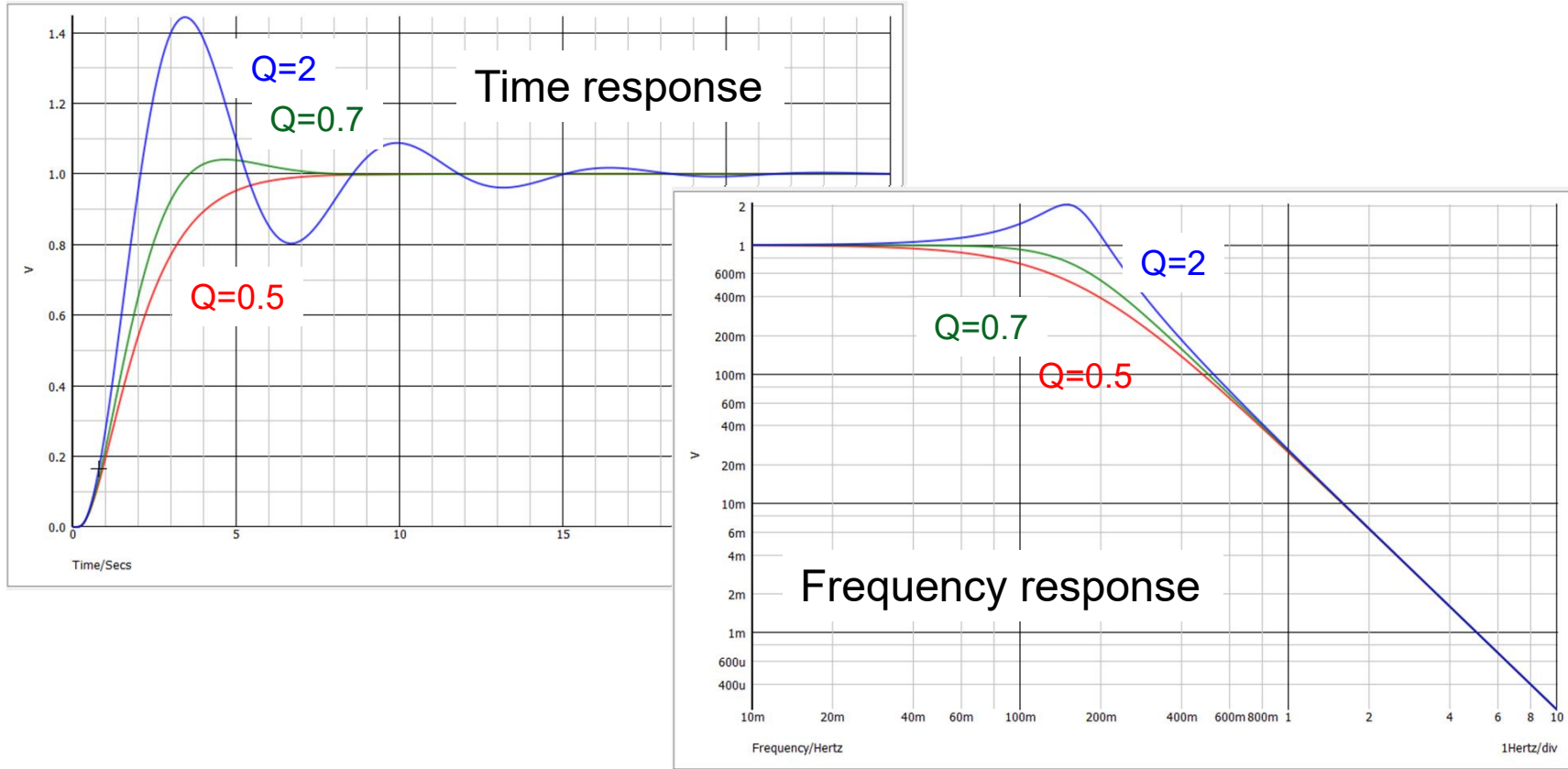
### 3. 2<sup>nd</sup> order circuits: optimal phase margin




- Optimal response → best trade-off between time and frequency response
- Obtained for (see details in appendix B):

$$Q = \frac{\sqrt{2}}{2} \leftrightarrow p_2 = 2A_0Fp_1 \leftrightarrow \varphi_M \approx 60^\circ$$
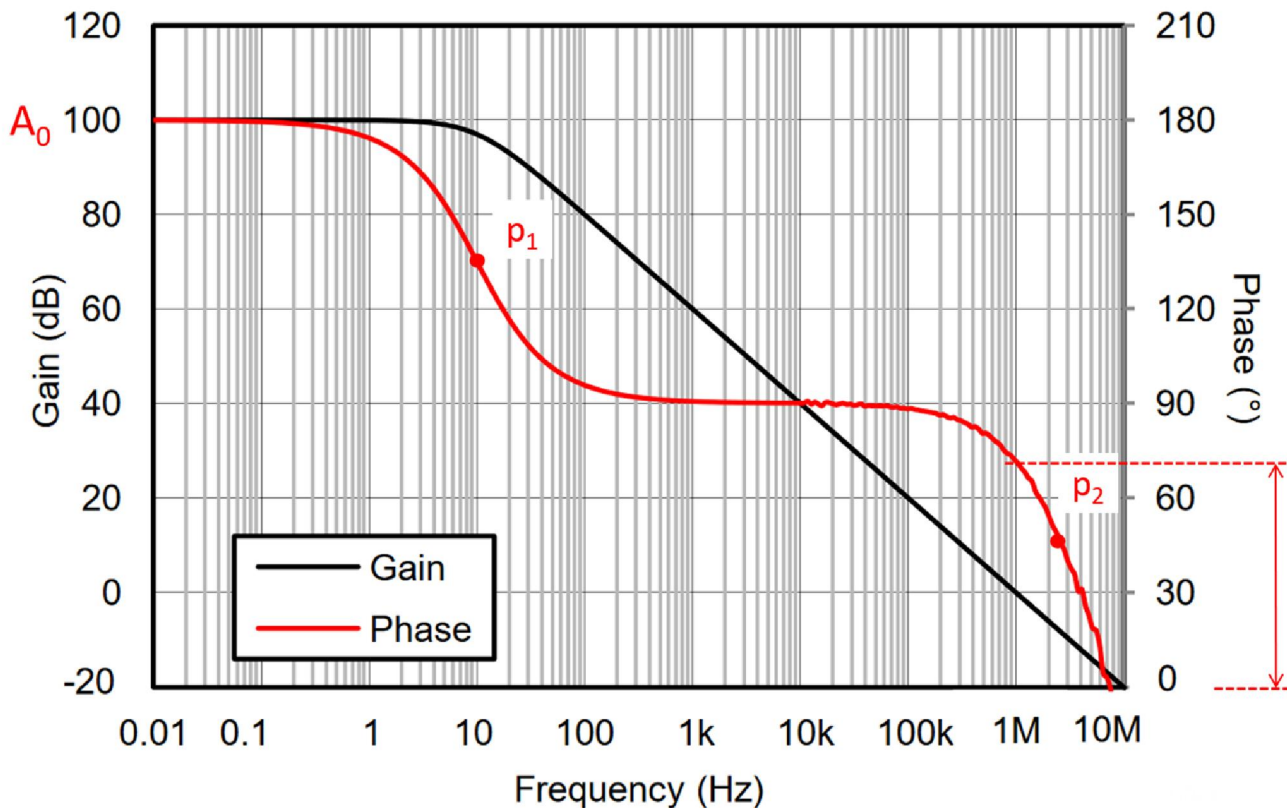
### 3. 2<sup>nd</sup> order circuits: unity-gain stable OPA

- Worst case for stability: the voltage follower ( $G = 1$ )
- Corollary: if an OPA is stable for  $G=1$ , it is also for any other practical value of  $G$
- **WARNING: all OPAs are not unity-gain stable**



$$A_0 = 100\text{dB} \rightarrow 10^5 \text{ } v/v$$

$$p_1(@ - 45^\circ) \approx 10\text{Hz}$$

$$p_2(@ - 135^\circ) > 2\text{MHz}$$

$$p_2 > 2A_0p_1$$


(unity - gain stable)

$$\varphi_M \approx 60^\circ$$



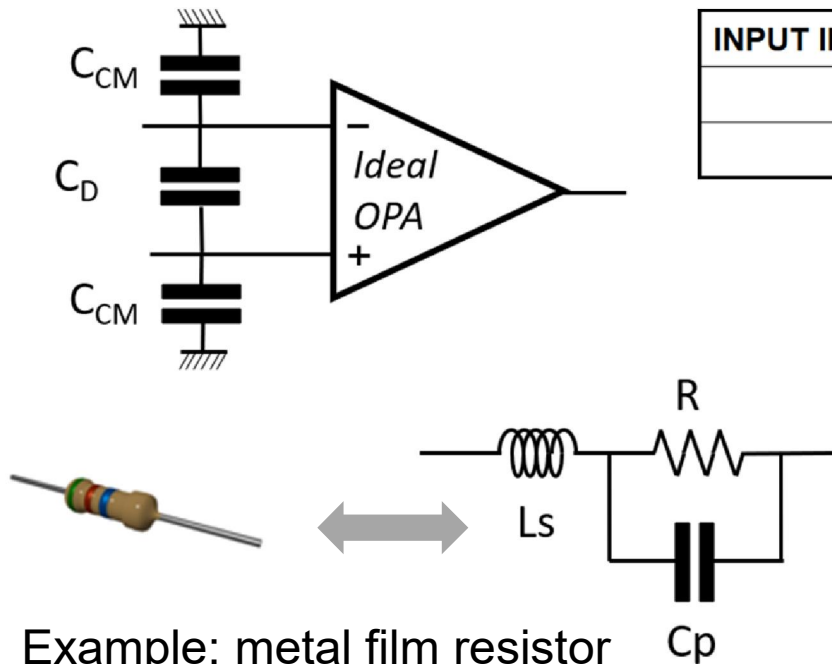
## 4. Higher order circuits: overview

- More than two poles → phase will cross  $-180^\circ$  → POTENTIAL UNSTABILITY
- OPAs are two-pole circuits, so where does the third pole come from?
  - Parasitic OPA capacitors
  - Stray capacitance of external components
  - Parasitic printed-circuit board (PCB) tracks capacitors



Example: metal film resistor  
 $R=1\text{M}\Omega$ ,  $L_s=5\text{nH}$ ,  $C_p=0.5\text{pF}$


INPUT IMPEDANCE Example: OPA1652		
Differential	$100 \parallel 6$	$\text{M}\Omega \parallel \text{pF}$
Common-mode	$6000 \parallel 2$	$\text{G}\Omega \parallel \text{pF}$

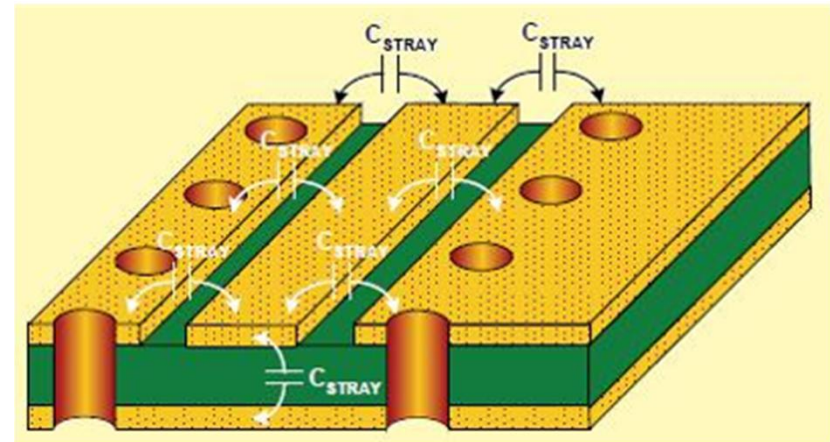

Example: FR4, 1.6mm thickness  
 $C_{STRAY} \approx 3\text{pF}/\text{cm}^2$



## 4. Higher order circuits: overview

- Oscillation occurs if  $|A(s) F| = 1$  and  $\varphi_{AF} = 0 \rightarrow$  what phase margin do we have?
- Stability analysis methodology:
  1. Include all parasitic components in the schematic, open the loop
  2. Isolate the F network, it will contain the parasitic components
  3. Determine the characteristics of the F network
  4. Determine at which frequency  $f_i$   $|A(s) F| = 1$

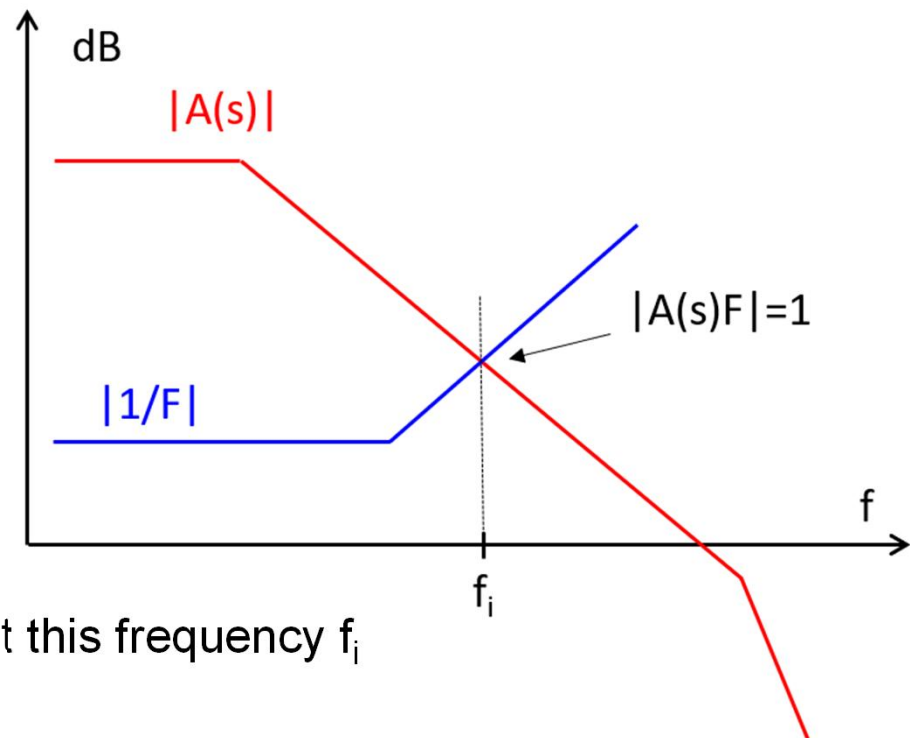


5. Determine phase margin at this frequency  $f_i$
6. Conclude on stability
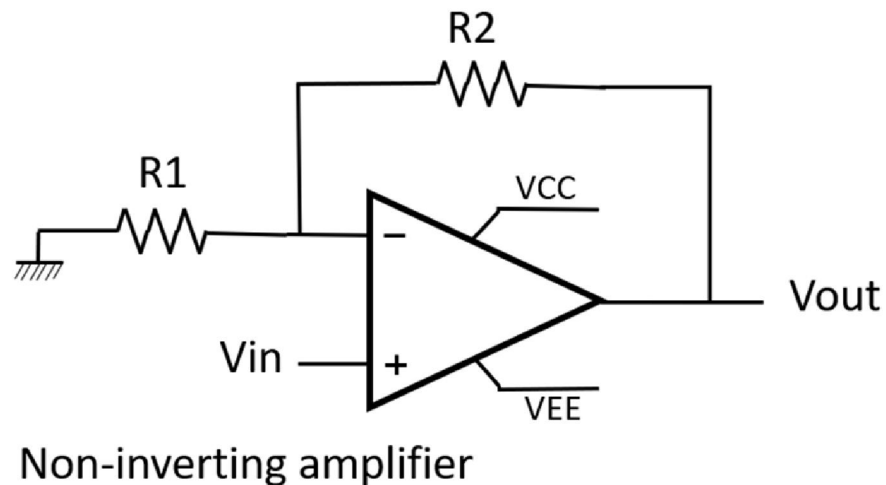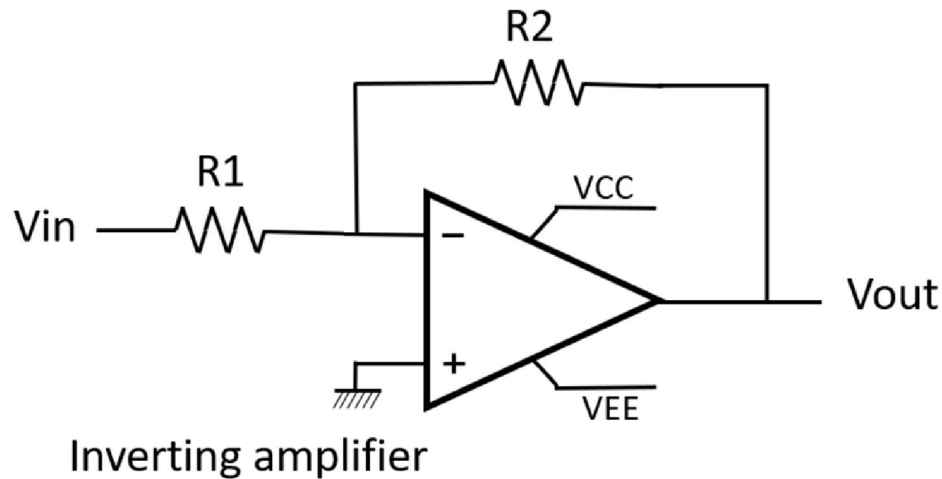
#### 4. Higher order circuits: Practical example 1: the inverting/non-inverting amplifier





No signal for stability analysis

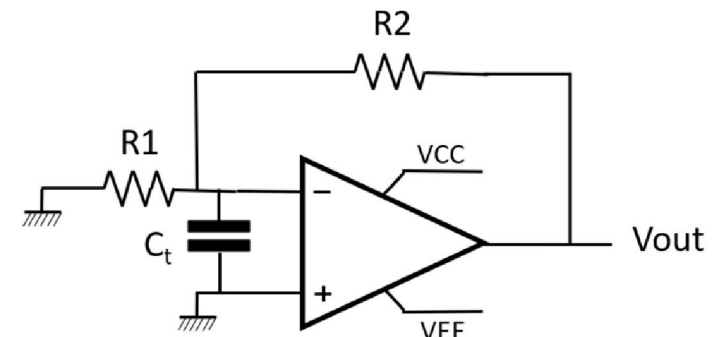

$$C_t = C_D + C_{CM-} + \sum \text{other parasitics} *$$

\*: parasitics due to printed-circuit board (PCB) traces among other things
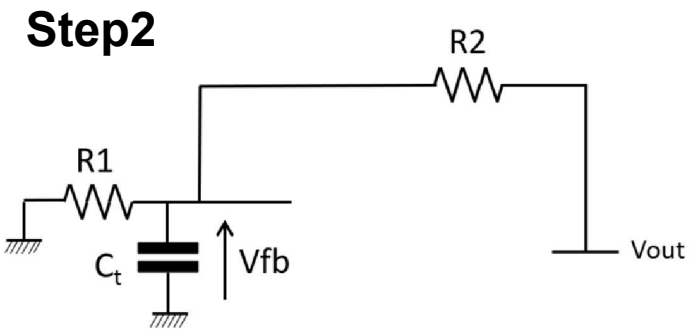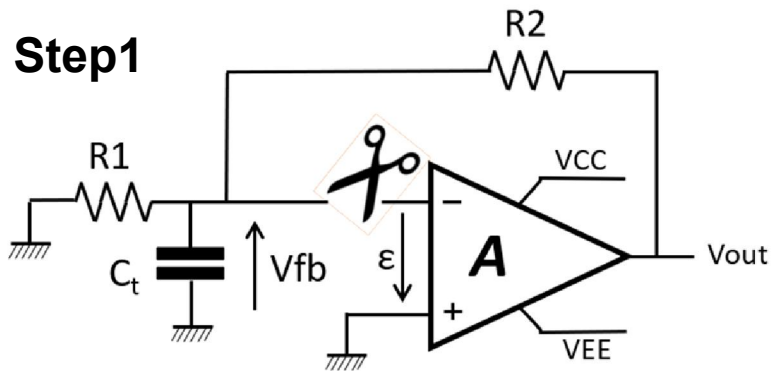
#### 4. Higher order circuits: Practical example 1: the inverting/non-inverting amplifier



Example:

$R1 = 22k\Omega$

$R2 = 220k\Omega$

$C_t = 10pF$

OPA:

$A_0 = 80dB$

$GBW = 20MHz$

Unity-gain stable

$p_1 = 2kHz$

$p_2 > 40MHz$

**Step3**


$$F = \frac{V_{fb}}{V_{out}} = \underbrace{\frac{R1}{R1 + R2}}_{F_0} \underbrace{\frac{1}{1 + (R1 || R2)C_t s}}_{p_F}$$

$$F_0 = \frac{1}{11}$$

$$p_F = \frac{1}{2\pi(R1 || R2)C_t} \approx 796kHz$$

#### 4. Higher order circuits: Practical example 1: the inverting/non-inverting amplifier

##### Step4

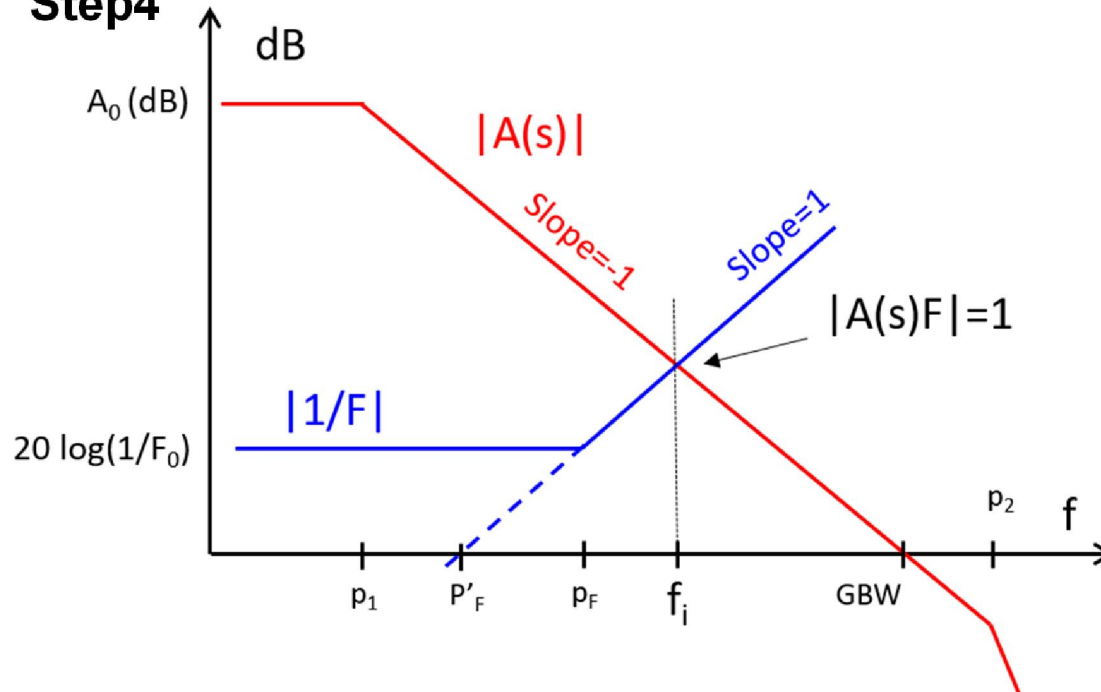

Because both slopes equal 1:

$$p'_F = p_F F_0 = 72.4 \text{ kHz}$$

$$\frac{f_i}{p'_F} = \frac{\text{GBW}}{f_i} \rightarrow f_i = \sqrt{p'_F \text{GBW}}$$




$$f_i = 1.2 \text{ MHz}$$

**Step5** Amplifier phase shift:  $\varphi_A = -90 - \tan^{-1} \frac{f_i}{p_2} = -93.4^\circ$

F block phase shift:  $\varphi_F = -\tan^{-1} \frac{f_i}{p_F} = -56.3^\circ$

$\varphi_M = (\varphi_A + \varphi_F) - (-180^\circ) = 37^\circ \rightarrow$  requires compensation  $\rightarrow$  Reduce R1, R2  
Reduce  $C_t$
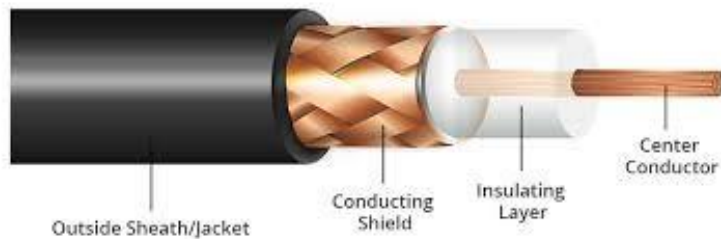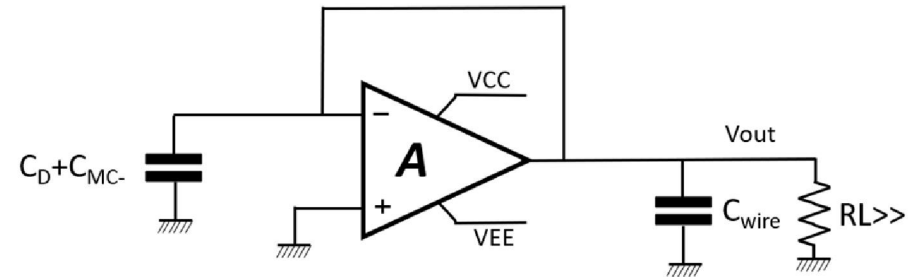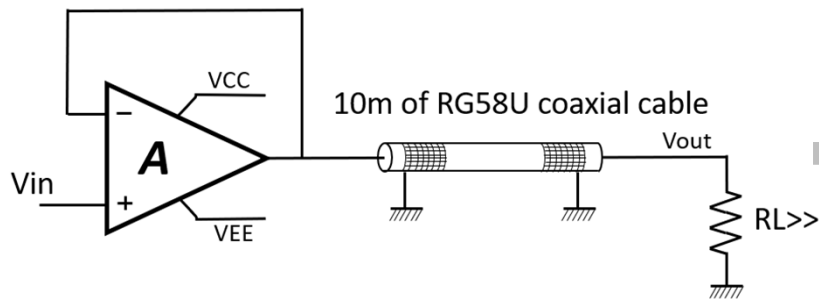
## 4. Higher order circuits: Practical example 2: the voltage follower




Example:  
RG58U  $\rightarrow C = 100\text{pF/m}$


$$C_{\text{wire}} = 10\text{nF}$$

## 4. Higher order circuits: Practical example 2: the voltage follower

### Step1

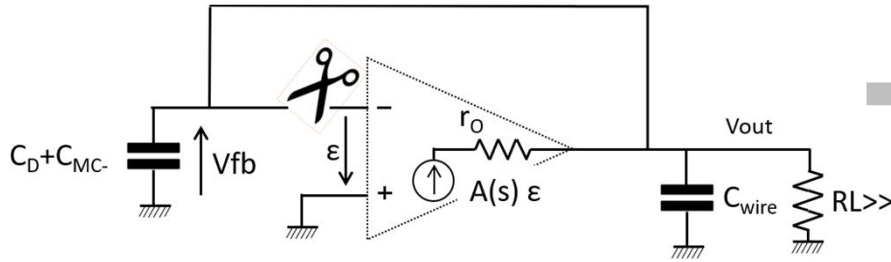

### Step2

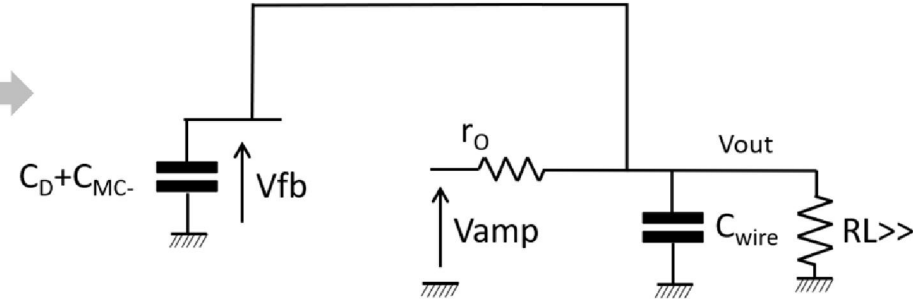

Example:

RG58U  $\rightarrow C = 100\text{pF/m}$

$C_{\text{wire}} = 1\text{nF}$

OPA:

$A_0 = 80\text{dB}$

$\text{GBW} = 20\text{MHz}$

Unity-gain stable

$r_o = 50\Omega$

$C_D + C_{MC-} = 10\text{pF}$

$p_1 = 2\text{kHz}$

$p_2 > 40\text{MHz}$

### Step3

$$F = \frac{V_{fb}}{V_{amp}} = \underbrace{\frac{RL}{r_o + RL}}_{F_0} \underbrace{\frac{1}{1 + (r_o || RL)C_t s}}_{p_F}$$


$$C_t = C_D + C_{MC-} + C_{\text{wire}} \approx C_{\text{wire}}$$

$$F_0 \approx 1$$

$$p_F = \frac{1}{2\pi(r_o || RL)C_t} \approx 3,18\text{MHz}$$

#### 4. Higher order circuits: Practical example 2: the voltage follower

##### Step4

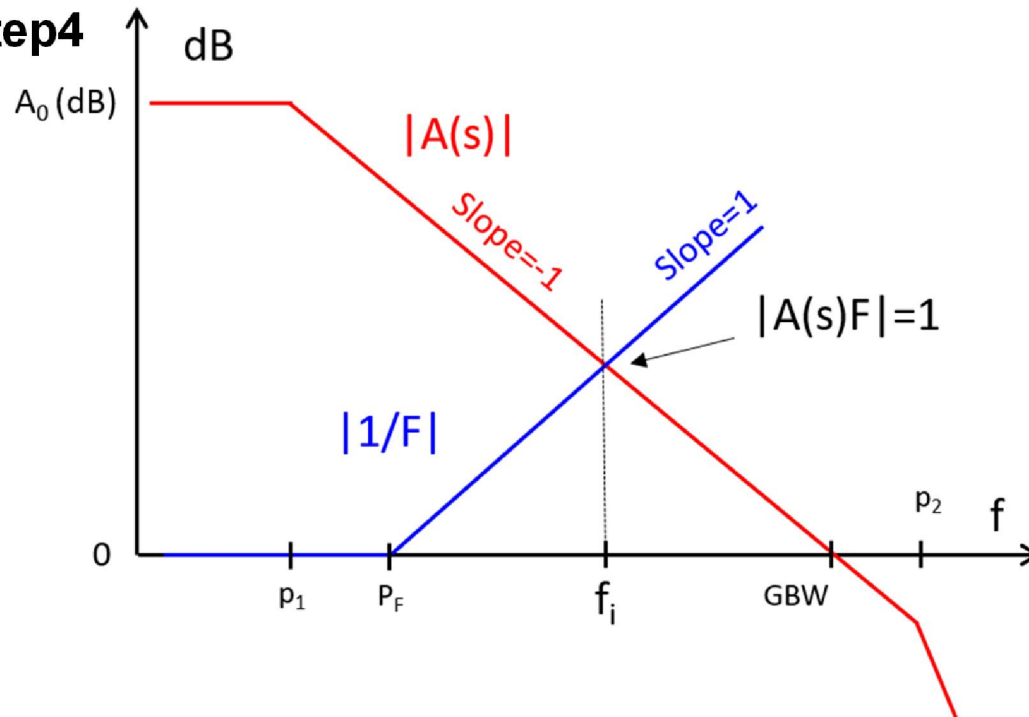

$$\frac{f_i}{p_F} = \frac{GBW}{f_i} \rightarrow f_i = \sqrt{p_F GBW}$$

$$f_i \approx 8\text{MHz}$$

##### Step5


Amplifier phase shift:  $\varphi_A = -90 - \tan^{-1} \frac{f_i}{p_2} = -101.3^\circ$

F block phase shift:  $\varphi_F = -\tan^{-1} \frac{f_i}{p_F} = -68.3^\circ$

$\varphi_M = (\varphi_A + \varphi_F) - (-180^\circ) \approx 10^\circ \rightarrow$  requires compensation


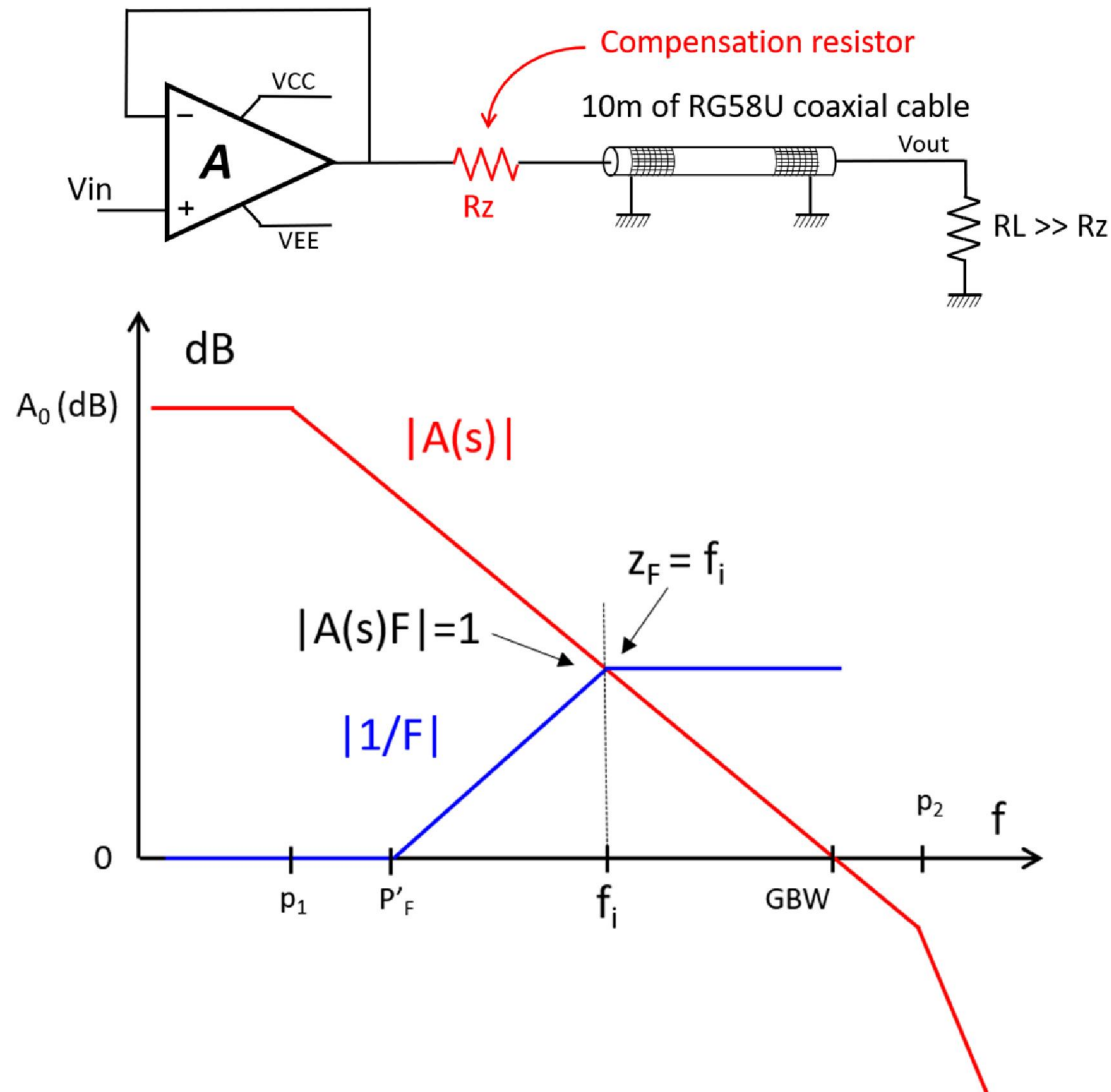
## 4. Higher order circuits: Practical example 2: the voltage follower



Now:

$$F = \frac{V_{fb}}{V_{amp}} \approx \frac{\overbrace{R_z C_t s}^{z_F}}{1 + \underbrace{(r_0 + R_z) C_t s}_{p'_F}}$$

$$F_0 \approx 1$$

$$p'_F = \frac{1}{2\pi(r_0 + R_z)C_t}$$

$$z_F = \frac{1}{2\pi R_z C_t}$$


If  $z_F$  is set to the previous  $f_i$  value:

$$\varphi_M \approx 50^\circ$$

(see details in appendix C)

## 5. Oscillators: What for?




Example: the PIC18F45K20 clock circuit

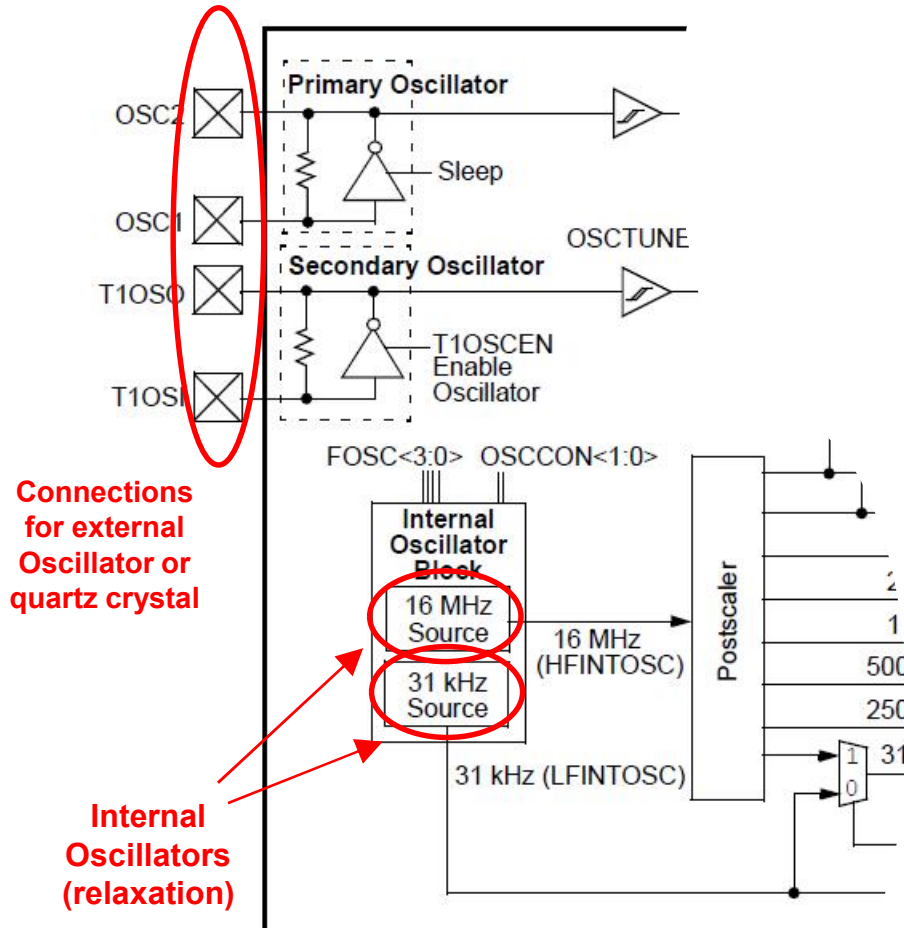


- Used whenever a signal with an accurate frequency value is required.
- Main features required:
  - Accurate frequency
  - Stable frequency
  - Spectral purity
  - Stable amplitude
- Two main techniques:
  - Relaxation oscillators
  - Harmonic oscillators
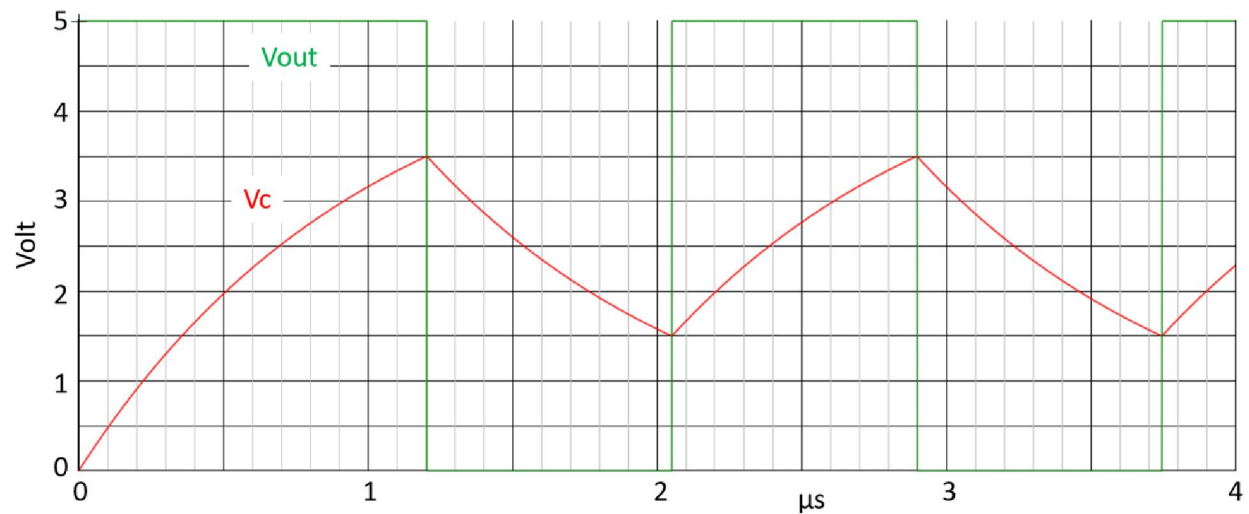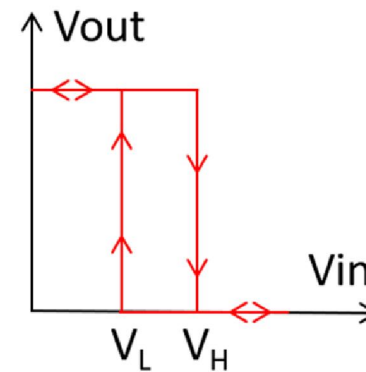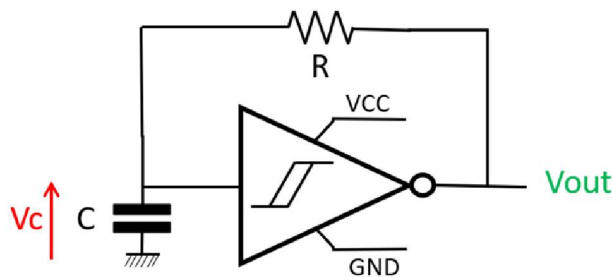
## 5. Oscillators: Relaxation oscillators

- Based on the charge and discharge of a capacitor between two known thresholds (comparator with hysteresis).
- Charge/discharge can be at constant voltage (exponential variation) or constant current (linear variation)


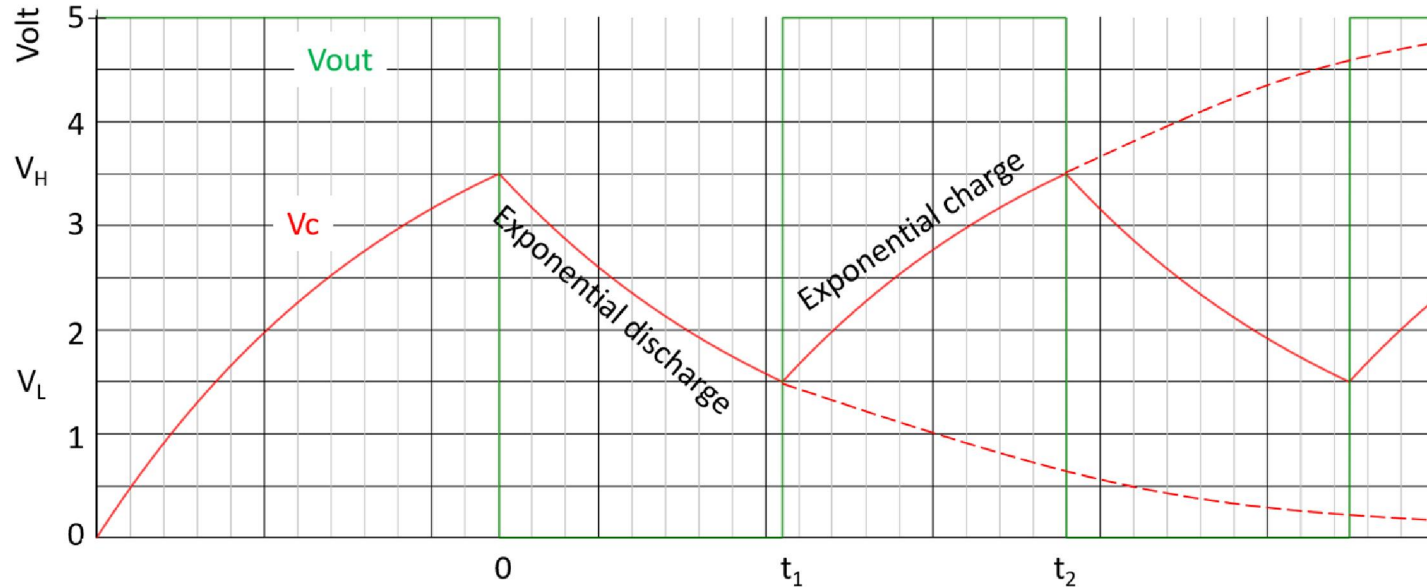
## 5. Oscillators: Relaxation oscillators



Discharge:  $V_L = V_H e^{\frac{-t}{RC}} \rightarrow t_1 = RC \ln \frac{V_H}{V_L}$




Charge:  $V_H - V_L = (V_{CC} - V_L)(1 - e^{\frac{-t}{RC}}) \rightarrow t_2 - t_1 = RC \ln \frac{V_{CC} - V_L}{V_{CC} - V_H}$

$$T = RC \left( \ln \frac{V_H}{V_L} + \ln \frac{V_{CC} - V_L}{V_{CC} - V_H} \right)$$


This example:  $1.695\mu\text{s}$  with  $R=1\text{k}\Omega$ ,  $C=1\text{nF}$

## 5. Oscillators: Relaxation oscillators

### Industrial circuit: the 555 timer

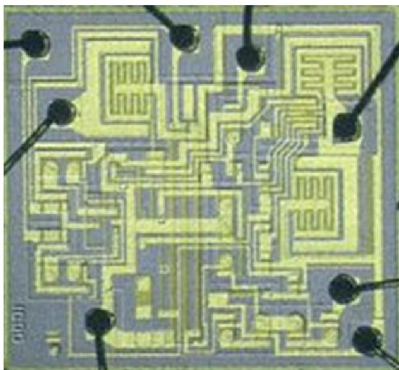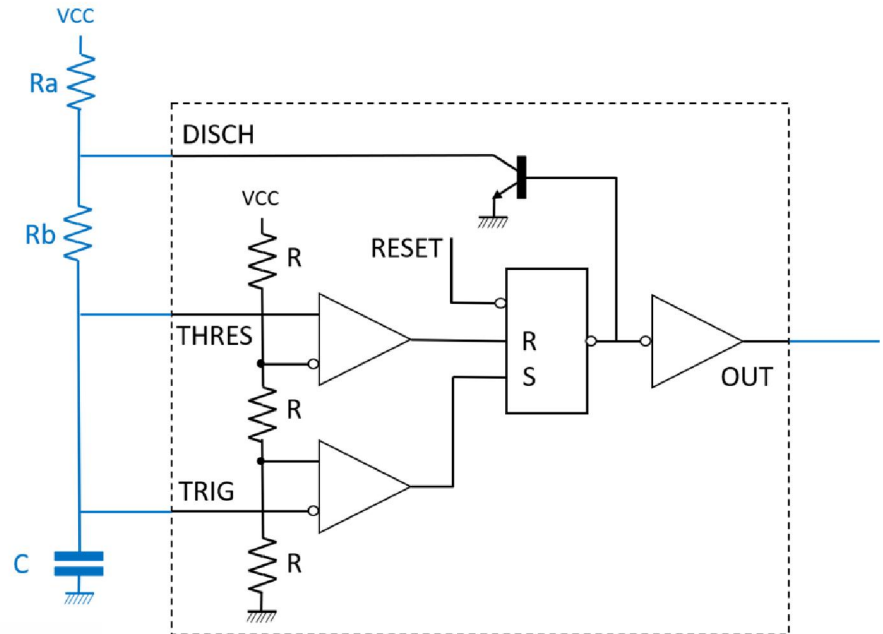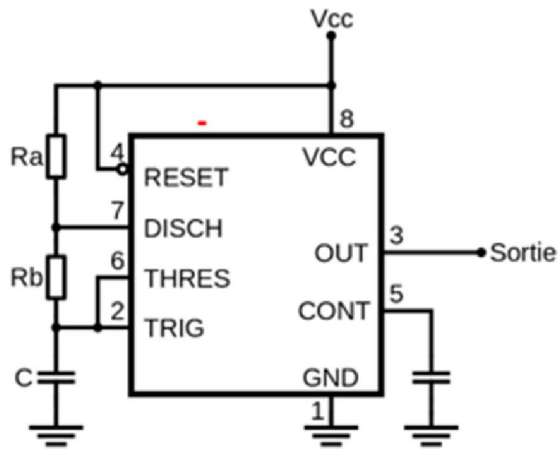

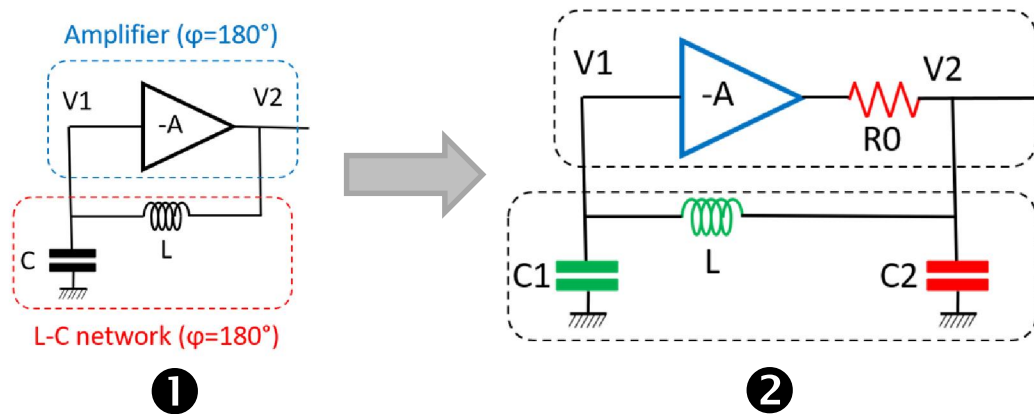
## 5. Oscillators: Harmonic quartz crystal oscillators






**2** Pierce Oscillator:  
an Extra phase shift due to R0  
ensure  $-180^\circ \rightarrow$  oscillation occurs  
at

$$f \approx \frac{1}{2\pi \sqrt{L \frac{C1C2}{C1 + C2}}}$$


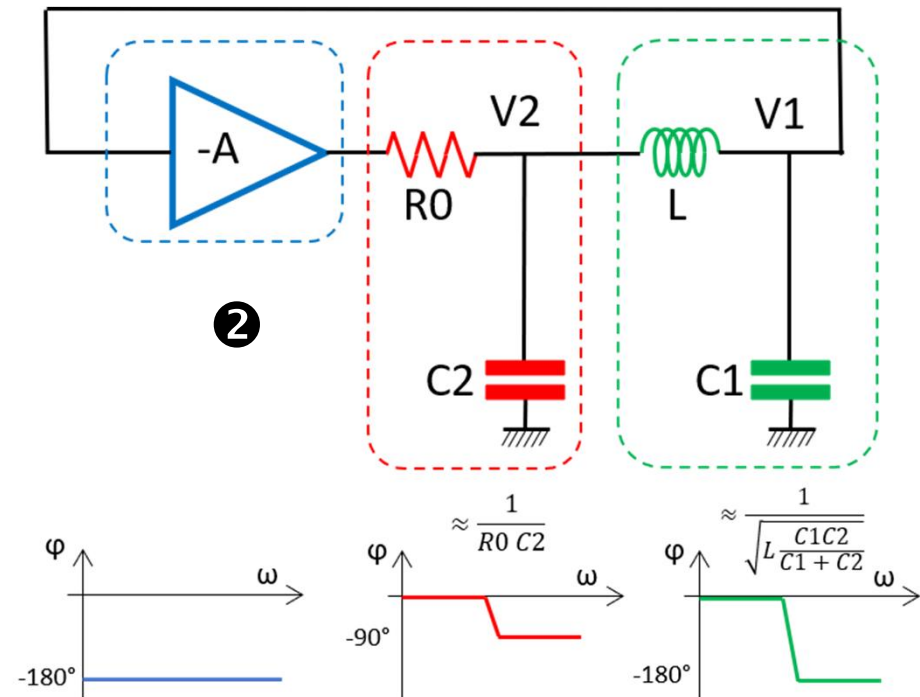
**1** Oscillator principle:  
the two phase shifts create  
positive feedback  $\rightarrow$  oscillation  
may exist if the gain A is large  
enough



## 5. Oscillators: Harmonic quartz crystal oscillators

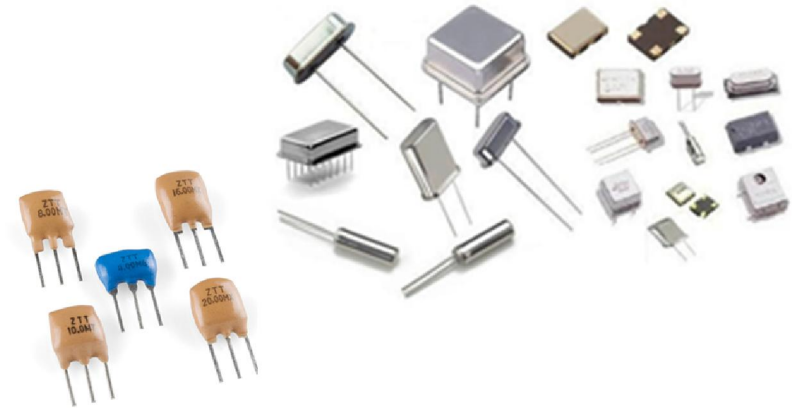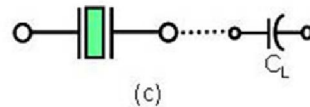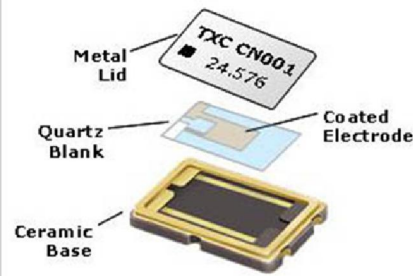



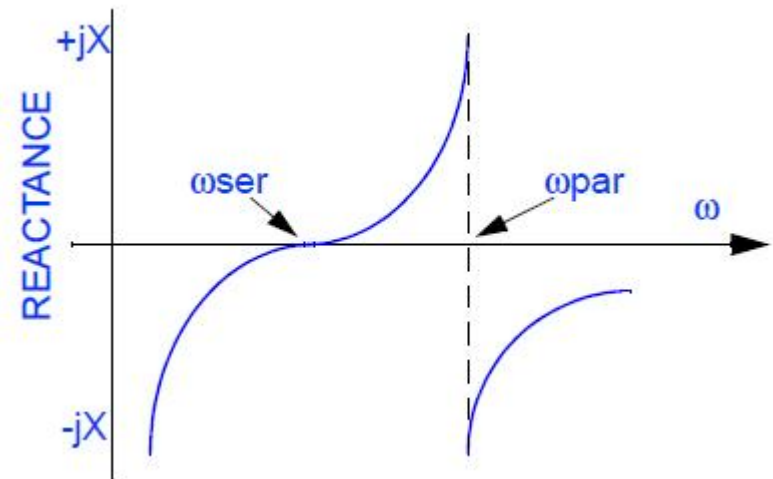
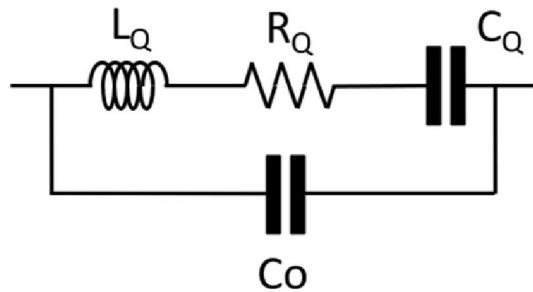
(Fig.7) (a) Metal can type resonator  
(b) Ceramic SMD type resonator  
(c) Symbol of crystal unit



$$\omega_{ser} = \frac{1}{\sqrt{L_Q C_Q}}$$

$$\omega_{par} = \omega_{ser} \sqrt{1 + \frac{C_Q}{C_o}}$$
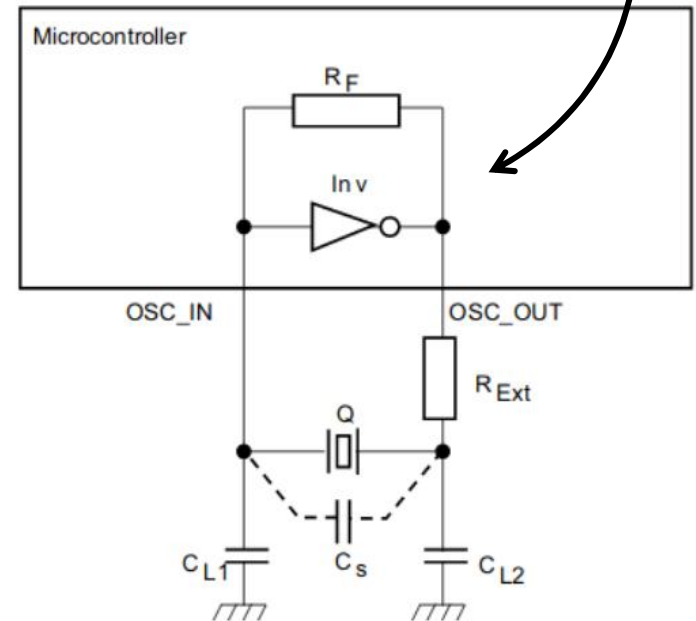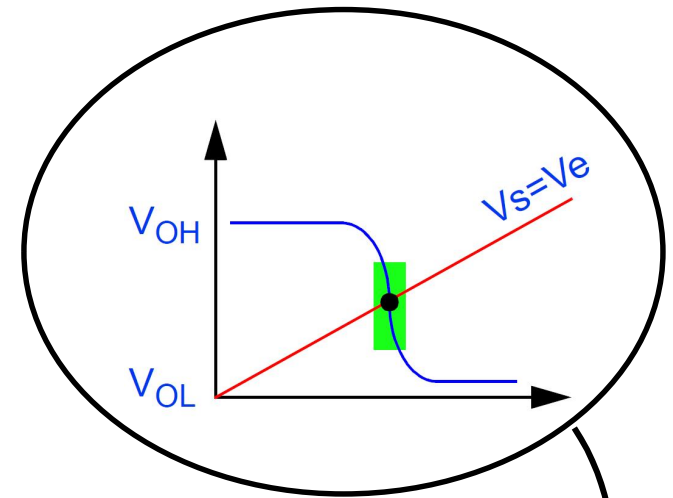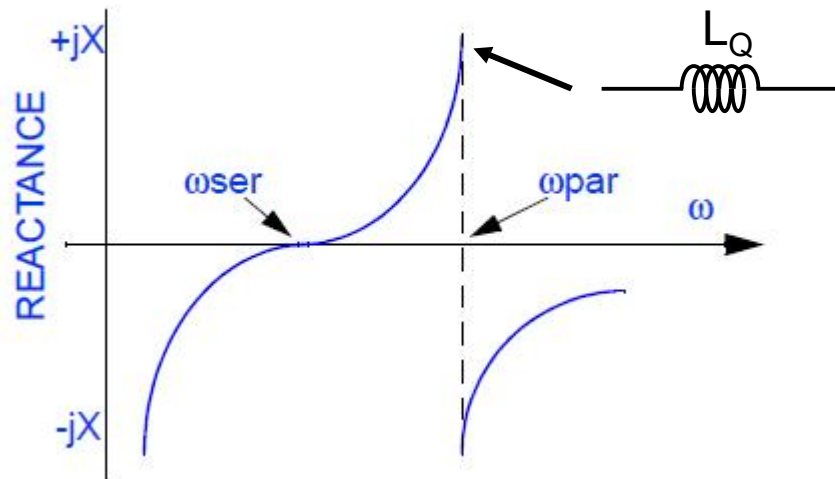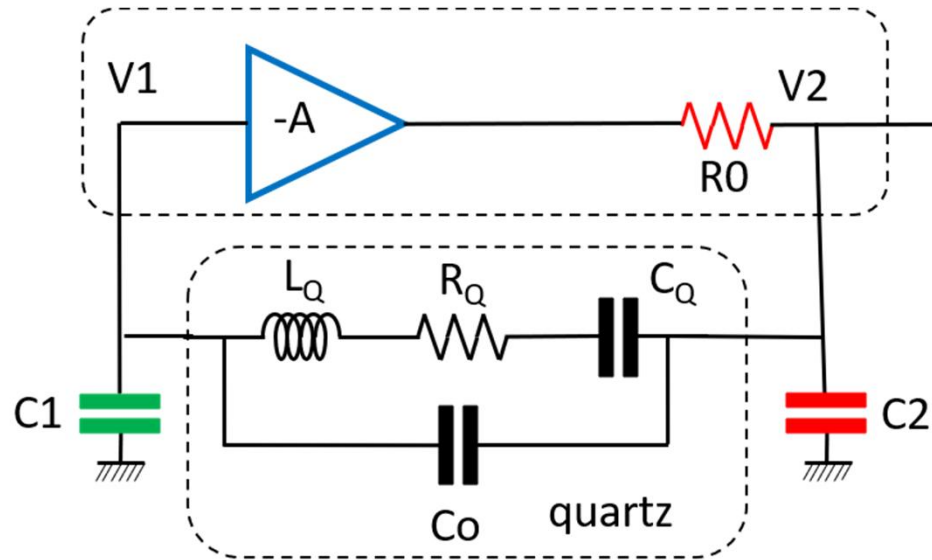
## 5. Oscillators: Harmonic quartz crystal oscillators





## 6. Appendix A: closed-loop poles of 2<sup>nd</sup> order circuits

$$H(s) = \frac{Ho}{s^2 + \frac{\omega_0}{Q} + \omega_0^2}$$


Normalized with  $\omega_0 = 1$ :

Normalized with  $\omega_0 = 1$ : 
$$H(s) = \frac{Ho}{s^2 + \frac{1}{Q} + 1}$$

Open-loop poles:  $p_1$  and  $p_2$

Closed-loop poles  $p'_1$  and  $p'_2$  are given by:
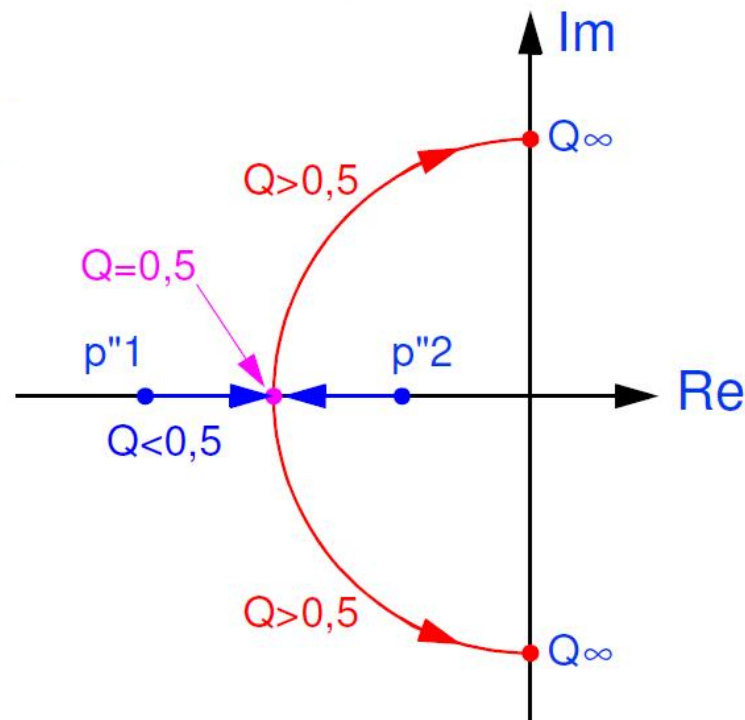
$$s^2 + \frac{1}{Q} + 1 = 0 \rightarrow p'_{1,2} = \frac{1}{2Q} \pm \frac{\sqrt{\frac{1}{Q^2} - 4}}{2}$$



## 7. Appendix B: optimal phase margin in 2<sup>nd</sup> order circuits

Open-loop poles:  $p_1$  and  $p_2$

$$H(s) = \frac{A_o}{1 + A_o F} = \frac{(1 + A_o F) p_1 p_2}{\underbrace{(1 + A_o F) p_1 p_2}_{\omega_0^2} + \underbrace{s(p_1 + p_2)}_{\frac{\omega_0}{Q}} + s^2}$$

The optimal response is obtained when:  $Q^2 = \frac{\omega_0^2}{(p_1 + p_2)^2} = \frac{(1 + A_o F) p_1 p_2}{(p_1 + p_2)^2} = \frac{1}{2}$

And thus:  $p_2 \approx 2 A_o F p_1$  if  $|p_1| \ll |p_2|$


So,  $p_2 \approx 2 A_o F p_1$  is the **condition that must be fulfilled** to obtain an optimal circuit response

For  $p_2 \approx 2 A_o F p_1$ , the -3dB bandwidth is  $\omega_{-3dB} = \sqrt{2} A_o F p_1$  which is 1,4 times larger than the 1<sup>st</sup> order circuit -3dB bandwidth. It is worth noting that it is achieved at neither expense in circuit complexity nor power consumption.

## 7. Appendix B: optimal phase margin in 2<sup>nd</sup> order circuits

Phase margin when  $p2 \approx 2 A_o F p1$ : open-loop study  $s_0 = j \omega_{0dB}$

$$T(s_0) = \frac{A_o F}{\left(1 + \frac{s_0}{p1}\right)\left(1 + \frac{s_0}{p2}\right)} \approx \frac{A_o F}{\left(\frac{s_0}{p1}\right)\left(1 + \frac{s_0}{p2}\right)} \quad \text{because } |p1| \ll |p2|$$

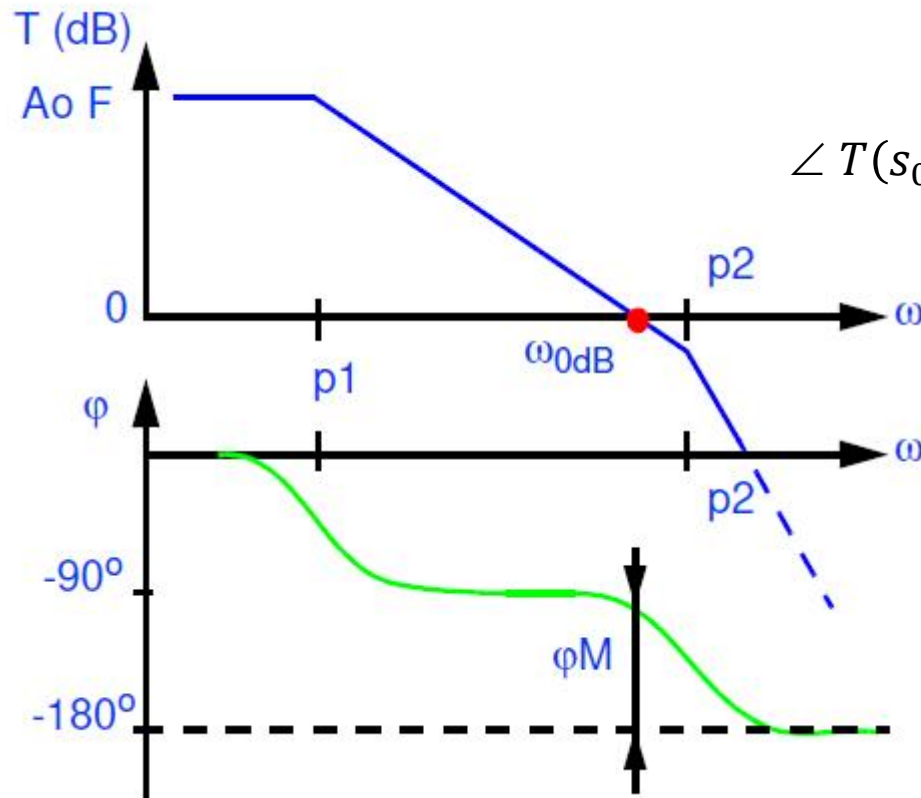

$$\omega_{0dB} \approx A_o F p1$$

$$\angle T(s_0) = -180^\circ + \phi_M = -90^\circ + \tan^{-1} \frac{A_o F p1}{p2}$$

$$\frac{p2}{p1} = \frac{A_o F}{\tan(90^\circ - \phi_M)}$$


For  $p2 \approx 2 A_o F p1$ :

$$\phi_M = 63.4^\circ \approx 60^\circ$$
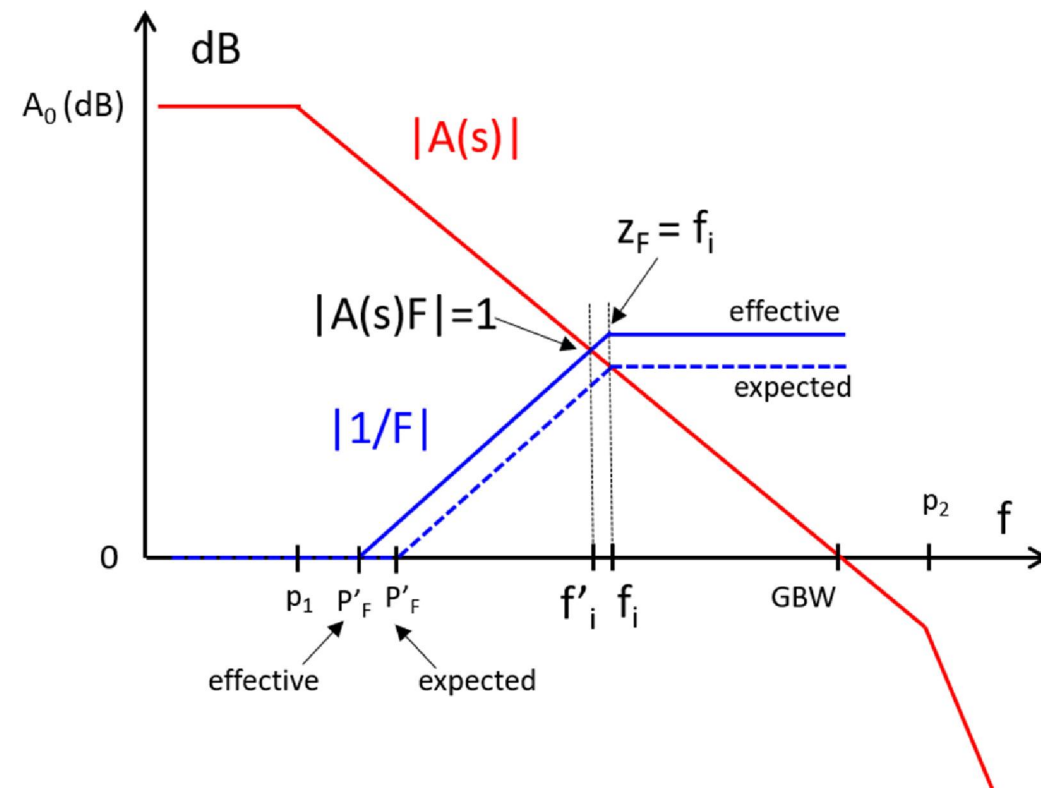
## 8. Appendix C: voltage follower compensation

Assume that  $z_F$  is set to the previous value of  $f_i \rightarrow R_Z = \frac{1}{2\pi z_F C_t} \approx 20\Omega$

Therefore,  $p'_F = \frac{1}{2\pi(r_0 + R_Z)C_t} \approx 2.3\text{MHz} \rightarrow$  the situation is not as expected:



$$f'_i = \sqrt{p'_{F\text{effective}} \text{GBW}} \approx 6.8\text{MHz}$$

Amplifier phase shift:

$$\varphi_A = -90 - \tan^{-1} \frac{f'_i}{p_2} \approx -99.6^\circ$$

F block phase shift:

$$\varphi_F = -\tan^{-1} \frac{f'_i}{p'_F} + \tan^{-1} \frac{f'_i}{z_F} \approx -31^\circ$$

$$\varphi_M = (\varphi_A + \varphi_F) - (-180^\circ) \approx 50^\circ$$

$\rightarrow$  nearly optimal