

ANALOG CIRCUITS DESIGN


AE2: Operational Amplifiers I,
OPA Basic concepts & circuits

Course overview

1. Basic concepts:
 - What is an operational amplifier? Why negative feedback?
 - OPAs work as expected as long as...
 - What does $\varepsilon = 0$ exactly mean?
 - Output impedance
2. Linear circuits:
 - The voltage amplifier
 - The voltage follower
 - The transresistance amplifier
3. Non-linear circuits: the comparator
4. How to choose an OPA:
 - Split-supply versus single supply
 - Output voltage limitation
 - Output current limitation
 - Offset voltage
 - Bias & offset currents
 - Small-signal bandwidth
 - Slew-rate

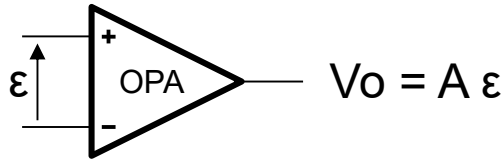
1. Basic concepts: What is an operational amplifier? Why negative feedback?

- What is an operational amplifier (OPA)?



It's basically a voltage amplifier with a very large voltage gain A

- What is negative feedback?

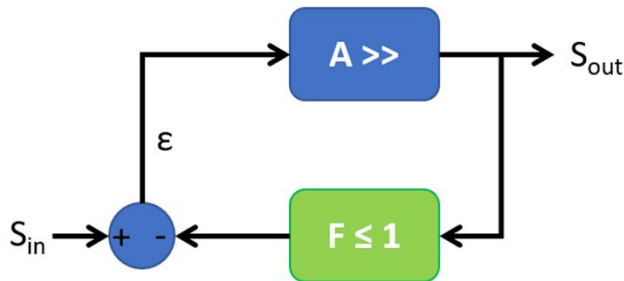

Negative feedback occurs when a fraction of the output signal S_{out} is subtracted from the input signal S_{in} so that error ε tends to zero.

$$\varepsilon = \frac{S_{out}}{A} = S_{in} - F S_{out}$$


$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + AF} \approx \frac{1}{F} \text{ if } AF \gg 1$$

- What does the OPA when used with negative feedback?

It only **attempts** to adjust its output voltage V_o so that $\varepsilon \rightarrow 0$

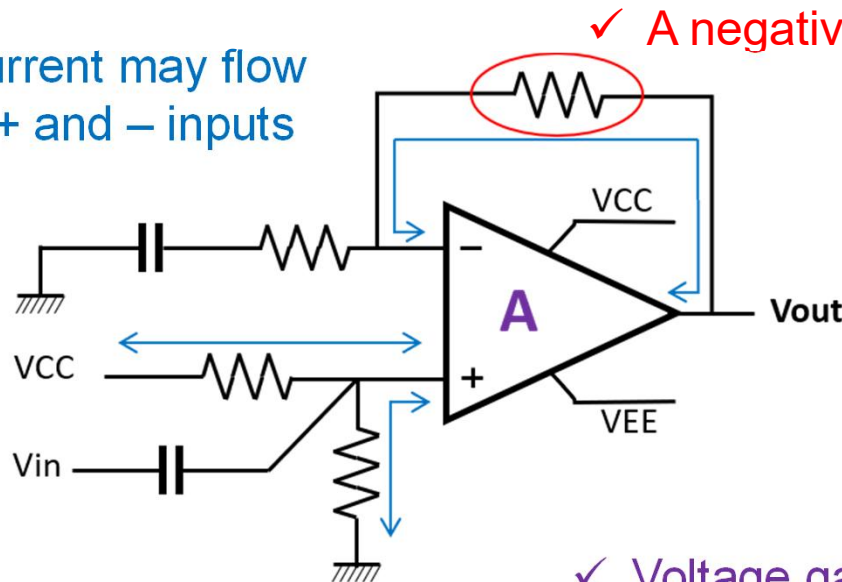1. Basic concepts: OPAs work as expected as long as ...

✓ A DC current may flow from/to + and - inputs



✓ A negative feedback path exists

✓ $V_{EE} \leq V_{out} \leq V_{CC}$
(linear operation)


✓ Voltage gain A remains sufficiently large

These four constraints must be **simultaneously** met

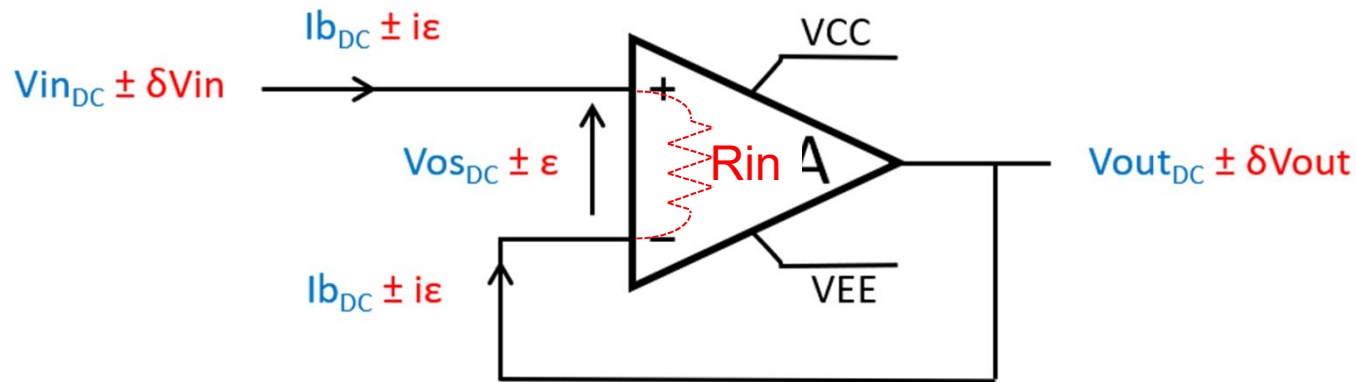1. Basic concepts: What does $\varepsilon = 0$ exactly mean?

➤ In normal operation, two modes are superimposed:

- Static (DC) mode (i.e. no signal applied)
- Dynamic (AC) mode (i.e. signal is applied at input)



I_{b_DC} : bias current
 V_{os_DC} : offset voltage } Expected to be zero but still existing due to OPA non-idealities


Linear operation $\leftrightarrow V_{EE} \leq V_{out_DC} \pm \delta V_{out} \leq V_{CC}$

OPA gain A is very large

$$\varepsilon = \frac{\delta V_{out}}{A} \rightarrow 0 \quad i_\varepsilon = \frac{\varepsilon}{R_{in}} \rightarrow 0$$

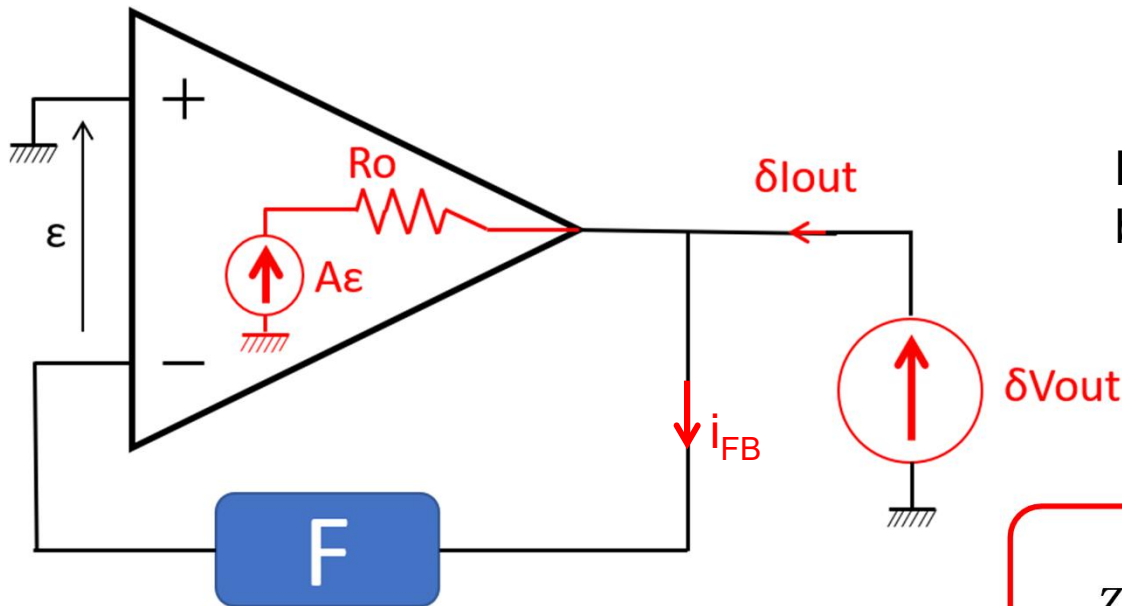1. Basic concepts: Output impedance

- OPA exhibits a non-zero output impedance R_o ($10\Omega \sim 50\Omega$ typically)



$$-\varepsilon = F \delta V_{out}$$

Let's now assume that i_{FB} can be neglected:


$$\delta V_{out} \approx A \varepsilon + R_o \delta I_{out}$$

$$Z_{out} = \frac{\delta V_{out}}{\delta I_{out}} \approx \frac{R_o}{1 + AF} \rightarrow 0$$

- The OPA can be viewed as a nearly ideal voltage source when feedback **senses the output voltage** (most of the circuits)

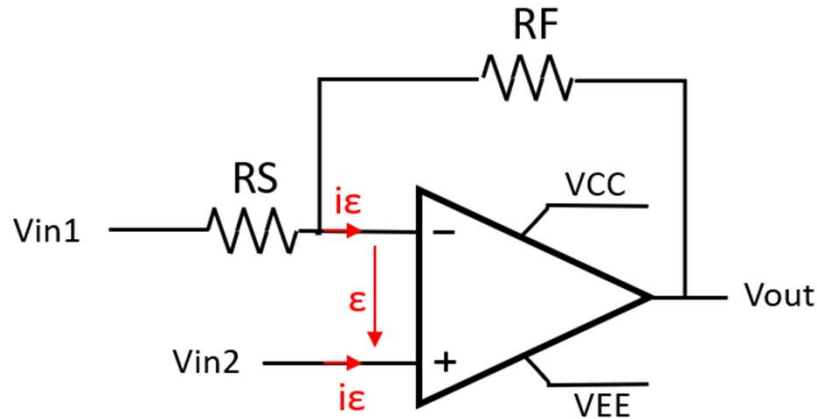2. Linear circuits: The voltage amplifier

➤ A circuit that you absolutely must know!



$$V_{out} = \frac{-R_F}{R_S} V_{in1} + \left(1 + \frac{R_F}{R_S}\right) V_{in2}$$

$$Z_{in1} = \frac{V_{in1}}{I_{in1}} = R_S$$


$$Z_{in2} = \frac{V_{in2}}{I_\epsilon} \rightarrow \infty$$

$$Z_{out} \approx 0$$

➤ Possible configurations:


- Inverting amplifier when $V_{in2}=0$
- Non-inverting amplifier when $V_{in1}=0$
- Differential amplifier
- Voltage follower when $R_F=0$ and $R_S \rightarrow \infty$

2. Linear circuits: The voltage follower

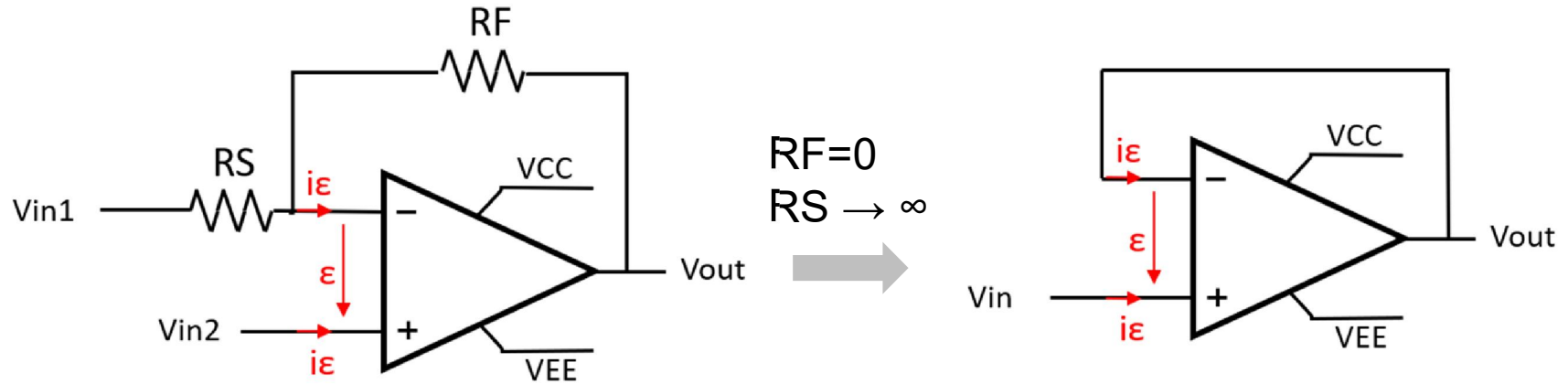


$$V_{out} = V_{in} \quad Z_{in} = \frac{V_{in}}{I_{\epsilon}} \rightarrow \infty \quad Z_{out} \approx 0$$

➤ Typically used as voltage buffer

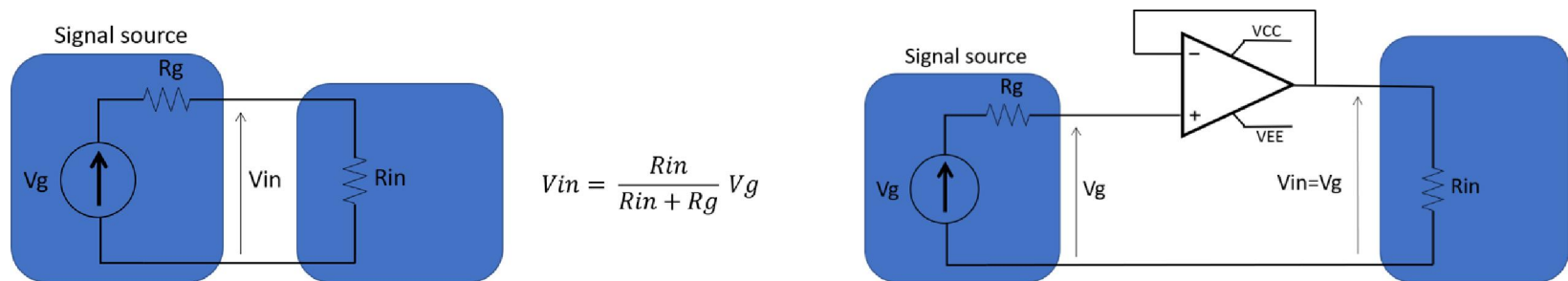

$$V_{in} = \frac{R_{in}}{R_{in} + R_g} V_g$$


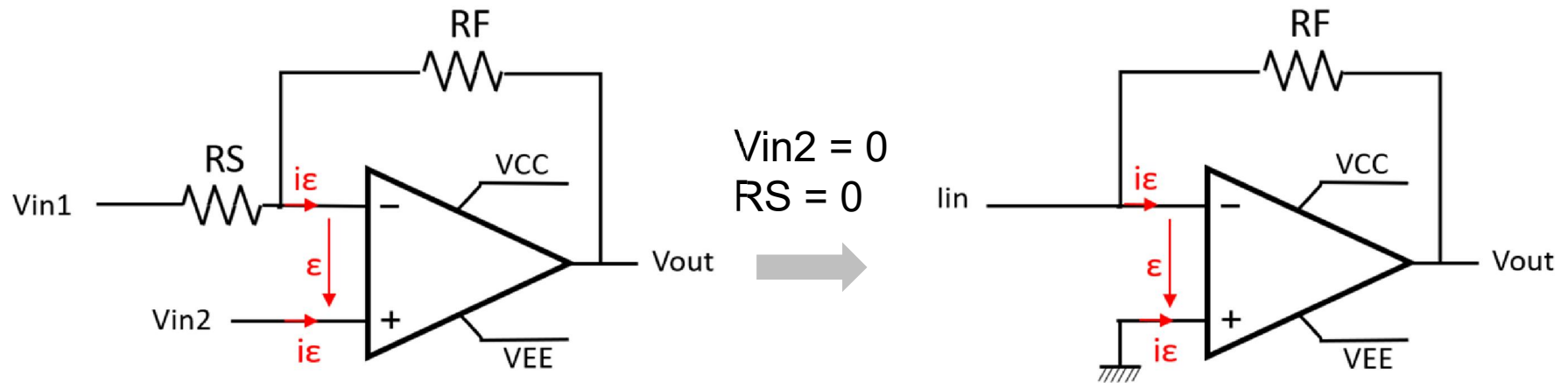
2. Linear circuits: The transresistance amplifier



$$V_{out} = -R_F I_{in} \quad Z_{in} = \frac{\epsilon}{I_{in}} \approx 0 \quad Z_{out} \approx 0$$

➤ Current-to-voltage converter


3. Non-linear circuits: The comparator

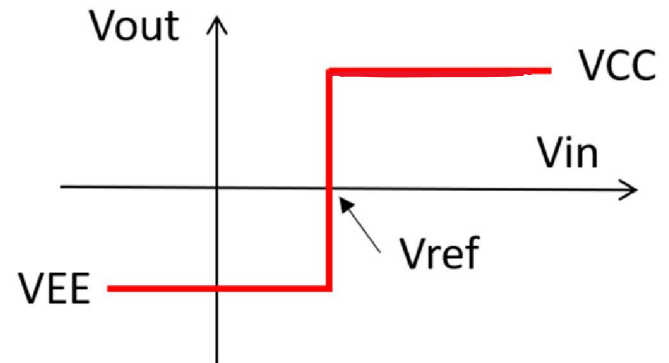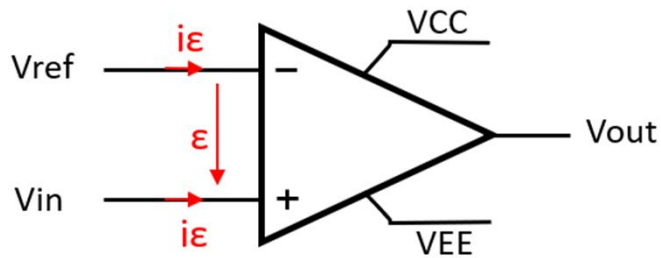


No feedback

Most of the time:
 $\varepsilon \neq 0$ and $i\varepsilon \neq 0$

➤ Problem with noisy signals

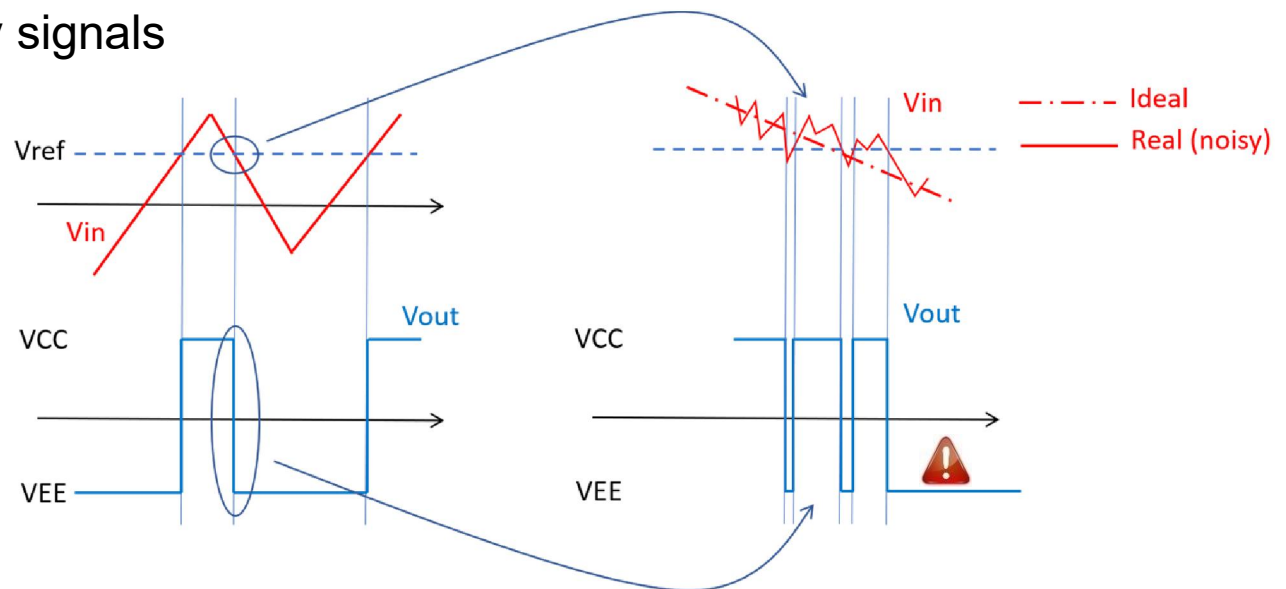

3. Non-linear circuits: The comparator

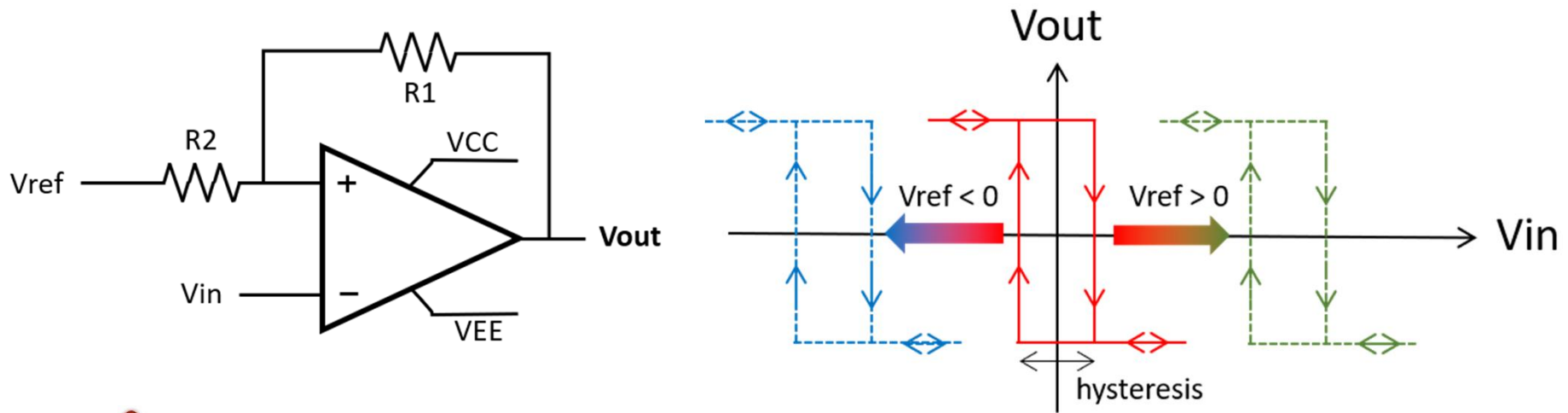

Positive feedback



Most of the time:
 $\varepsilon \neq 0$ and $i\varepsilon \neq 0$

➤ Hysteresis must be larger than noise



➤ Some OPA don't work properly as comparator → better use dedicated circuits

4. How to choose an OPA: Split-supply versus single supply

➤ Split-supply ($V_{EE} = -V_{CC}$)

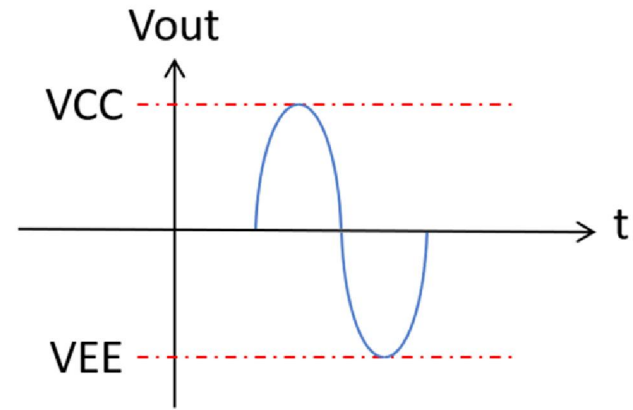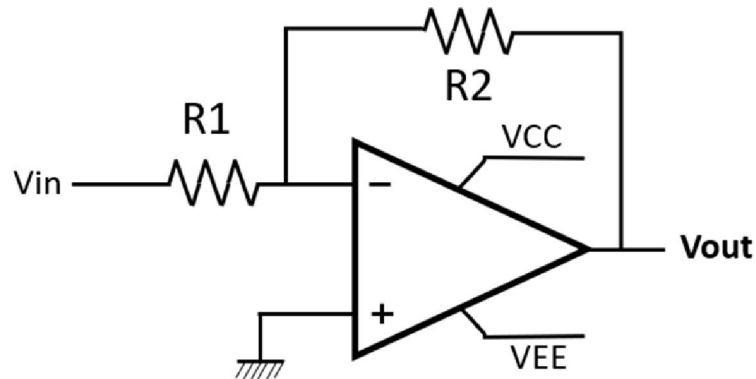

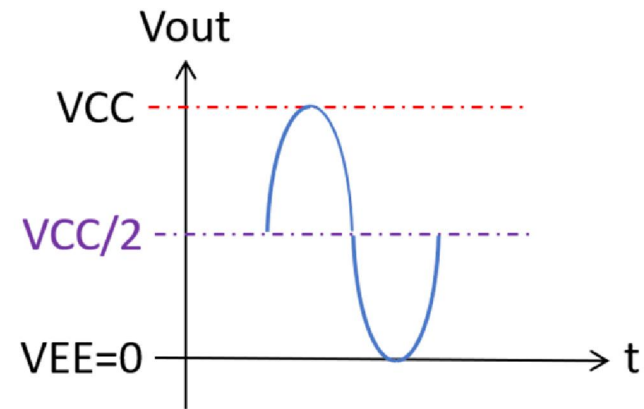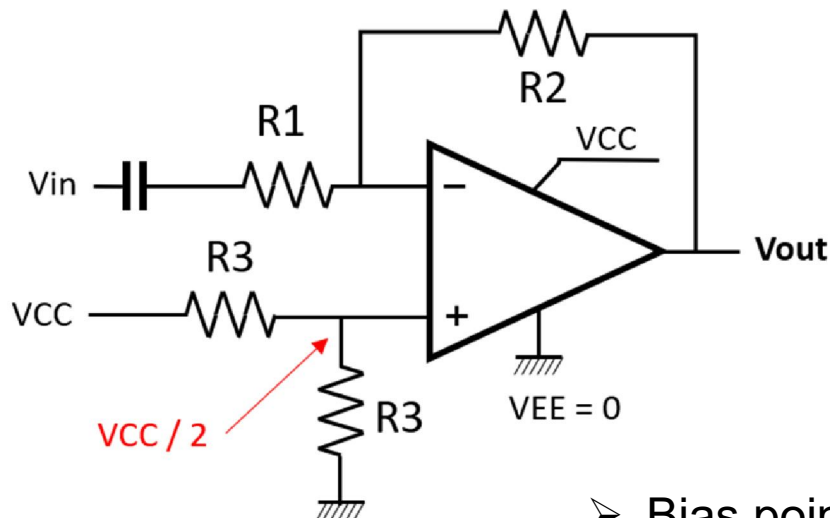
➤ Single supply ($V_{EE} = 0$) for battery-operated circuits




➤ Bias point automatically set to $V_{CC}/2$ (optimal value)

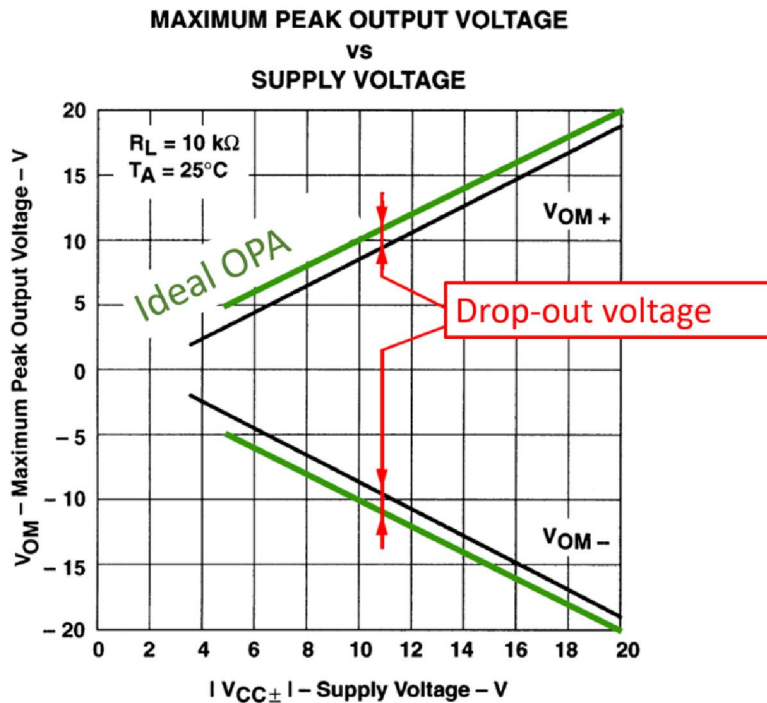4. How to choose an OPA: Output voltage limitation

- Ideally $V_{EE} \leq V_{out} \leq V_{CC}$, but drop-out limits output voltage
- Battery-operated circuits require low V_{CC} value → better use rail-to-rail OPA



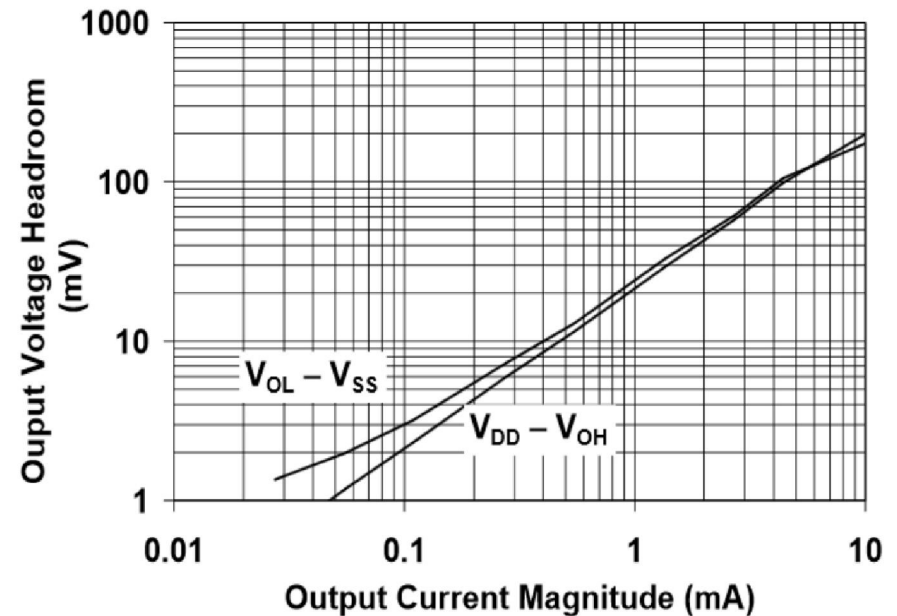
Drop-out is constant → increasing influence as supply voltage decreases




Drop-out greatly reduced but not eliminated

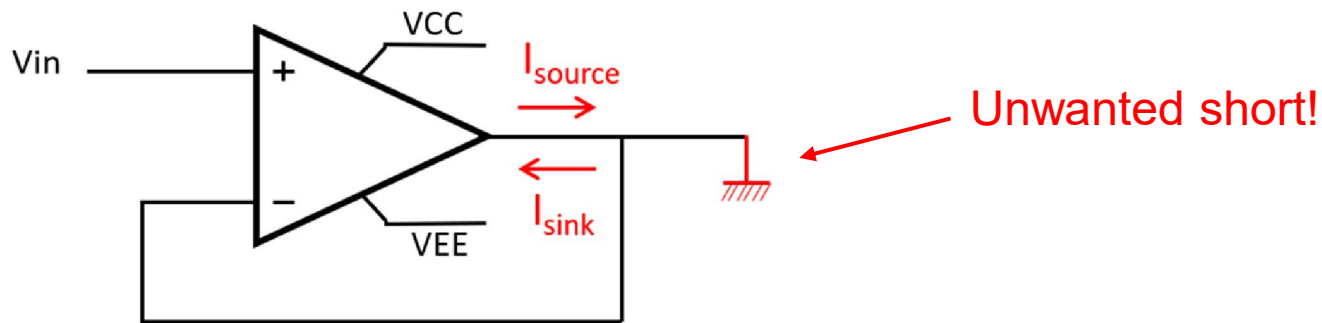4. How to choose an OPA: Output current limitation

- Output current is limited to protect OPA against circuit defects



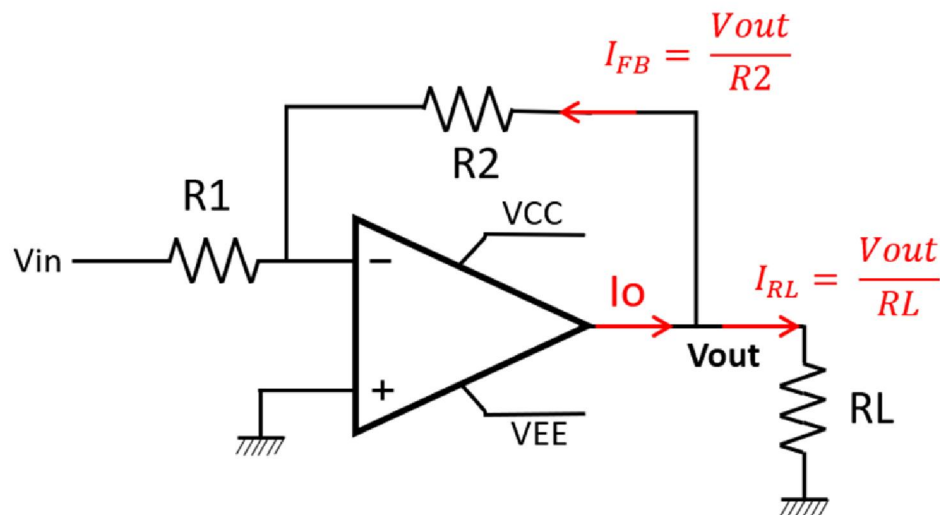- But output current limitation also applies in normal operation!





I_o is limited $\rightarrow I_{FB}$ should be minimized to save power for the load $\rightarrow R2$ should be large enough, but not too large to minimize noise

Standard OPA: $I_o \approx 20mA$

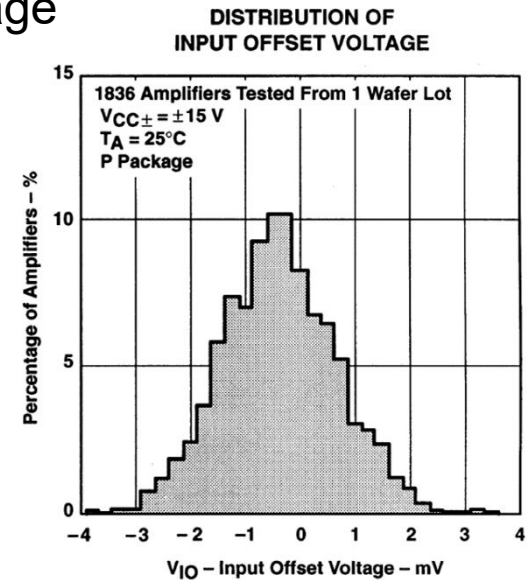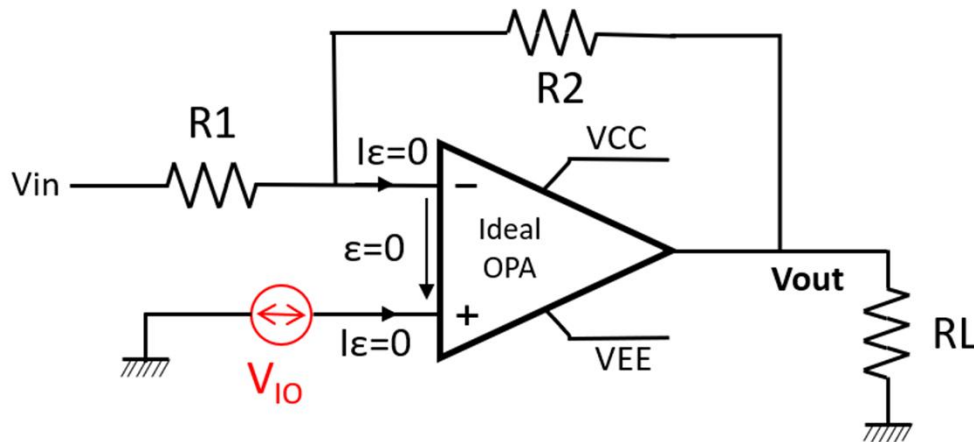4. How to choose an OPA: Offset voltage

- Random DC voltage due to asymmetry in OPA input stage
- Model: a DC voltage source added to an ideal OPA




$$V_{out} = \frac{-R2}{R1} V_{in} \pm \left(1 + \frac{R2}{R1}\right) V_{IO}$$

- It may be a problem:
 - For high gain and low supply amplifiers
 - For high resolution ADC drivers

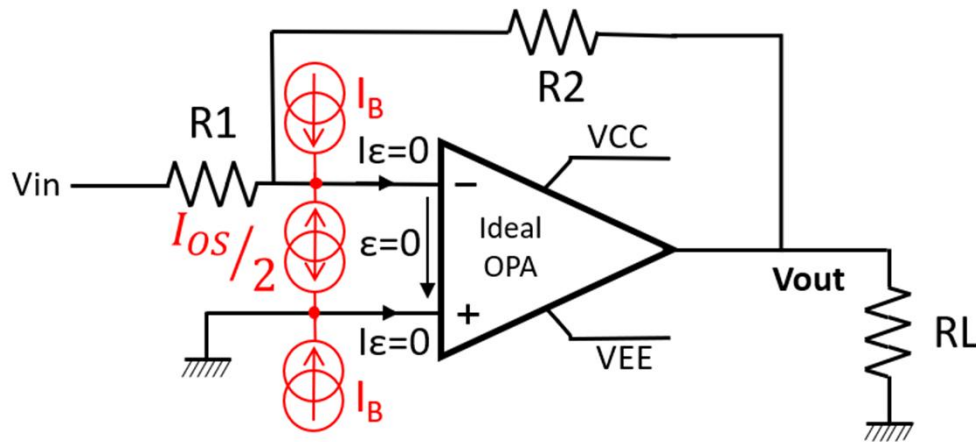4. How to choose an OPA: Bias & offset currents

- DC input currents necessary to operate the OPA input stage
- Model: three DC current sources added to an ideal OPA



Bias current: $I_B = \frac{I_{B+} + I_{B-}}{2}$
(usually known polarity)


Offset current: $I_{OS} = |I_{B+} - I_{B-}|$
(random polarity)

- It may be a problem:
 - For low signal currents
 - For high value of resistor $R2$

$$V_{out} = \frac{-R2}{R1} V_{in} \pm R2 I_B \pm R2 \frac{I_{OS}}{2}$$

Depends on polarity
Random

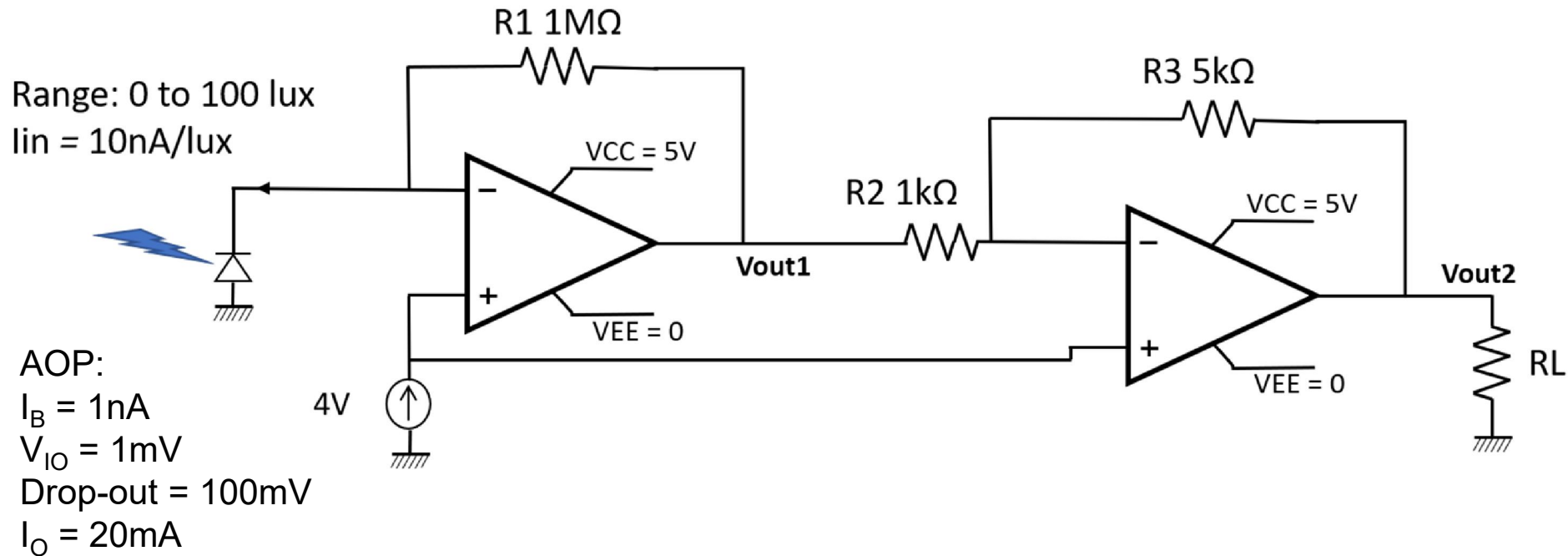4. How to choose an OPA: good or poor design?




	OK	KO
I_B		
V_{IO}		
Drop-out		
I_O		

	OK	KO
I_B		
V_{IO}		
Drop-out		
I_O		

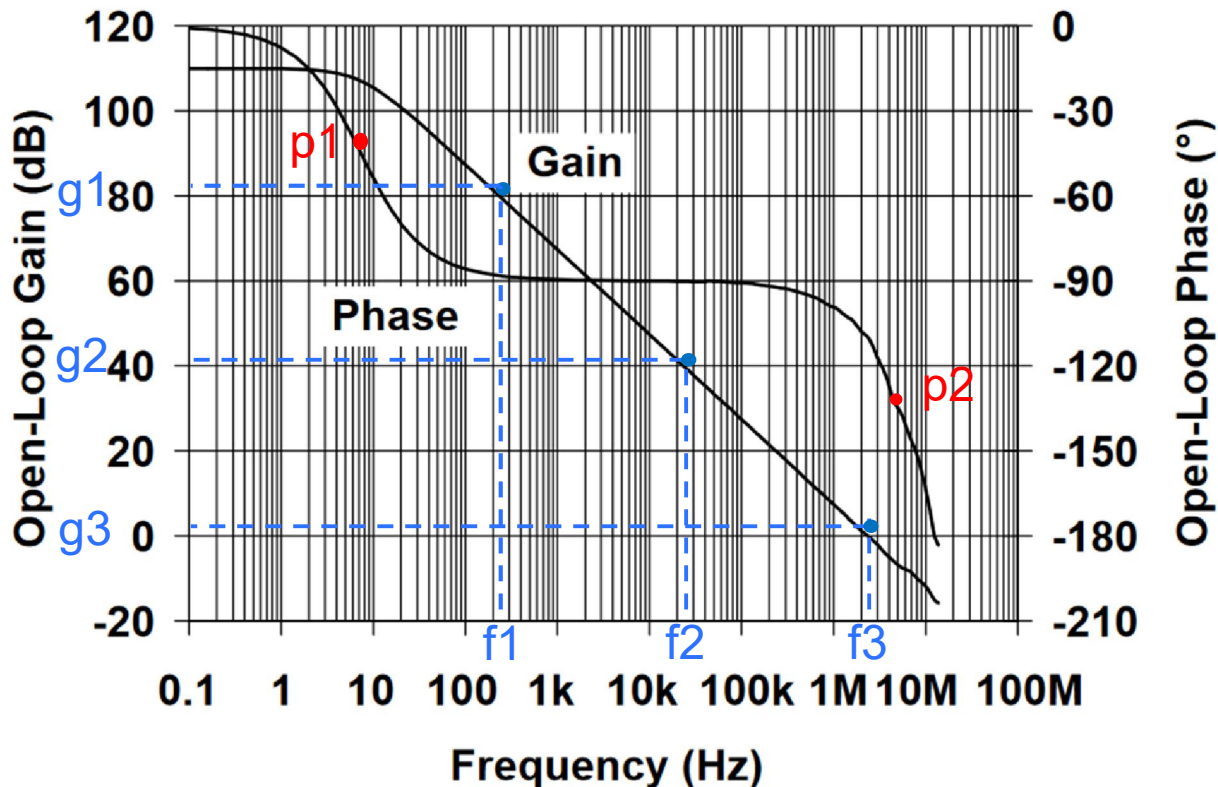4. How to choose an OPA: Small-signal bandwidth

- Amplifier's gain is not constant: at last, two poles exist (p1, p2)
- 1st order behaviour dominates in usable frequency range:
 - $GBW = \text{gain} \times \text{bandwidth} = \text{constant}$
 - $GBW = g_1 f_1 = g_2 f_2 = g_3 f_3$ (g_i are closed-loop gains)




Example: MCP6274
GBW = 2MHz

Gain=1 → BW=2MHz


Gain=10 → BW=200kHz

Gain=100 → BW=20kHz

4. How to choose an OPA: Slew-rate

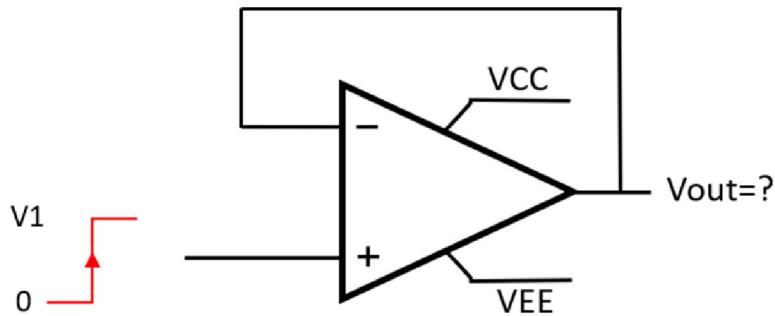

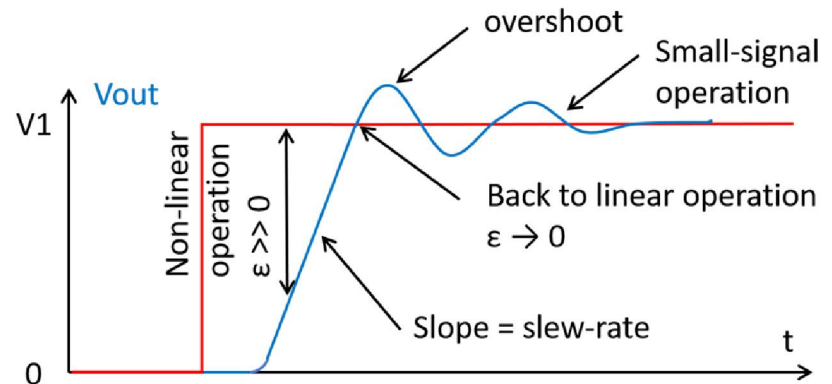➤ $\frac{dV_{out}}{dt}$ is limited \rightarrow slew-rate




➤ If $\frac{dV_{out}}{dt} > \text{slew-rate} \rightarrow$ signal is distorted

➤ Sinewave $A \sin(\omega t)$: $\left(\frac{dV}{dt}\right)_{\max} = 2 \pi f A$

➤ Slew-rate is a concern for large and/or high-frequency signals

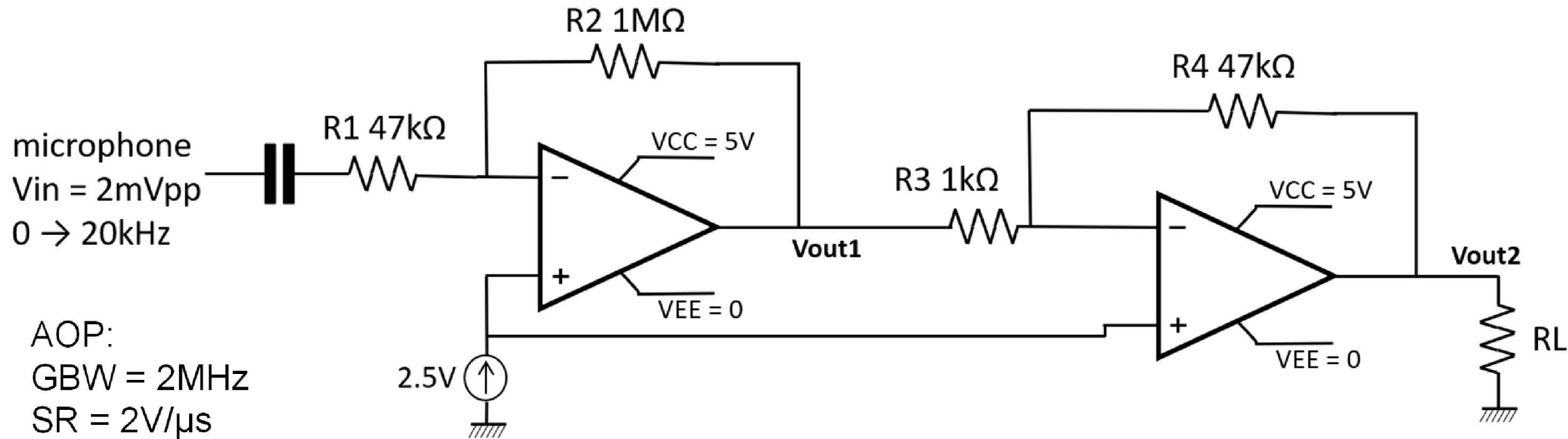4. How to choose an OPA: good or poor design?



	OK	KO
GBW		
SR		

	OK	KO
GBW		
SR		