

ANALOG CIRCUITS DESIGN


AE1: Basic analog-circuit equations

Course overview

1. Kirchoff's laws
2. Murphy's laws
3. Ground node is neither a black hole nor black magic
4. Series and parallel association of dipoles
5. Voltage source (Thevenin's model)
6. Current source (Norton's model)
7. Thevenin-Norton equivalence
8. Controlled sources
9. The voltage divider & the current divider
10. Superimposition
11. The concept of equivalent impedance

1. Kirchhoff's laws

➤ Kirchhoff's voltage law (KVL)

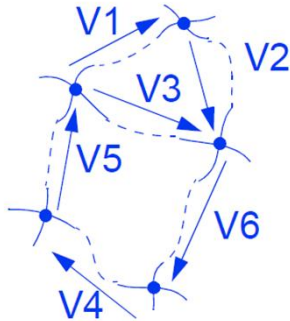


- ✓ In a loop, the sum of the voltages is zero


Some examples:

$$-V1 -V2 +V3 = 0$$

$$V5 + V4 + V6 + V3 = 0$$

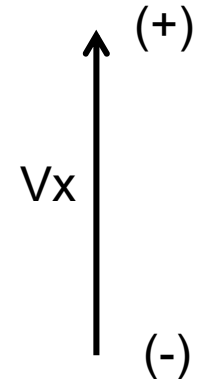

➤ Kirchhoff's current law (KCL)

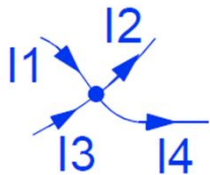

- ✓ At a node, the sum of the currents is zero

$$\text{example: } +I1 -I2 +I3 -I4 = 0$$

- ✓ Corollary: the sum of the inflows equals the sum of the outflows (no accumulation)
- ✓ Convention: the current entering a node is positive

2. Murphy's laws

Edward Aloysius Murphy Jr
1918-1990

American aerospace engineer who
worked on safety-critical systems



"Anything that can go wrong will go wrong"

"If anything simply cannot go wrong, it will anyway"

"If there is a possibility of several things going wrong,
the one that will cause the most damage will be the
one to go wrong"

3. Ground node is neither a black hole nor black magic

- What is ground?

The ground is a node that was arbitrarily chosen as the reference for voltage measurement in a circuit.

- What happens in the ground?



Nothing else than in any other node, the sum of currents is still zero

Corollary:



in the ground, currents do not disappear any more than they are generated

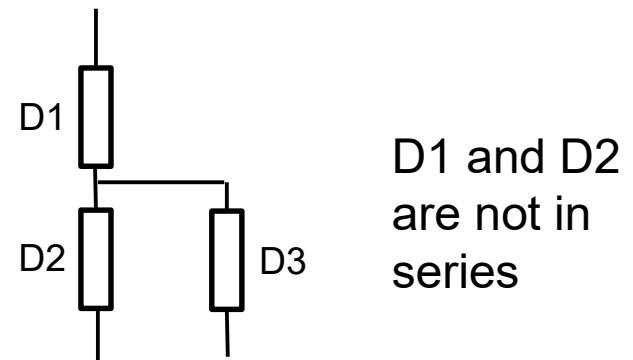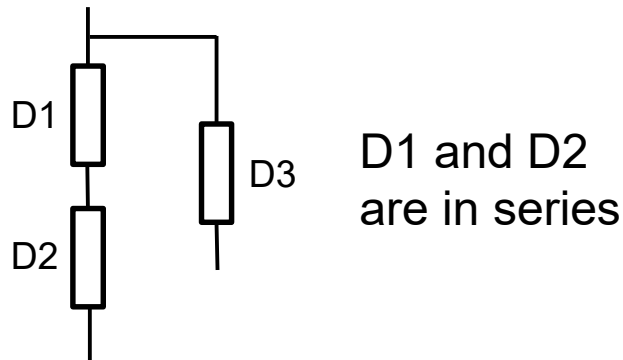4. Series and parallel association of dipoles



- Series association: one common node **not shared** with other dipoles, impedances add



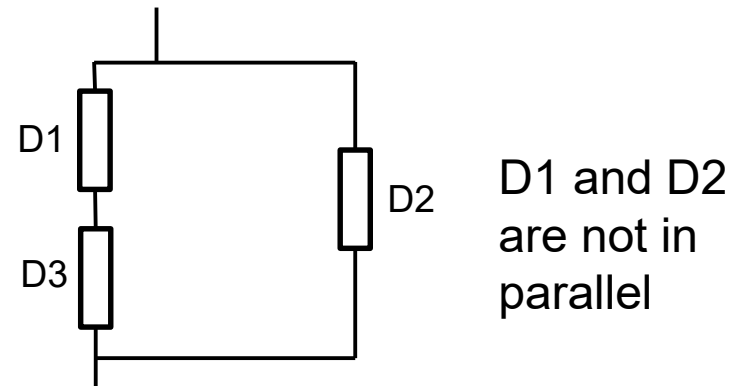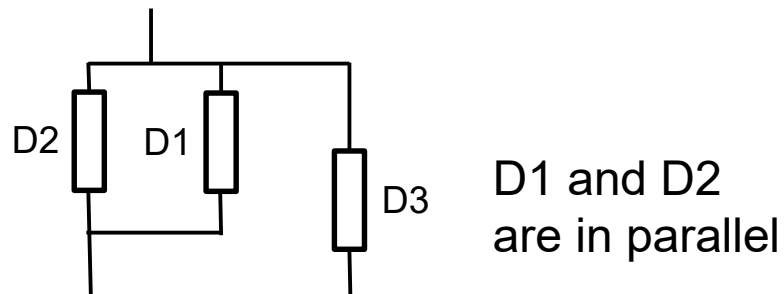- Parallel association: two nodes in common **possibly shared** with other dipoles, admittances add




5. Voltage source (Thevenin's model)

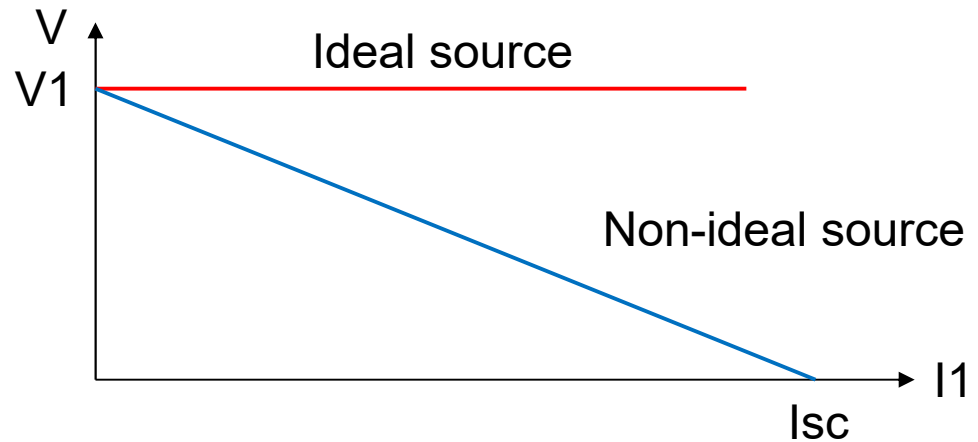
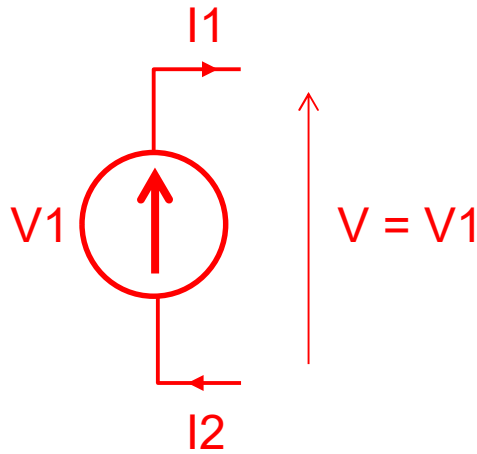


➤ Voltage source:

- $I1 = |I2|$
- Current may be positive, negative or zero
- $V1$: open-circuit voltage
- Isc : short-circuit current
- R : internal resistance (linear model)

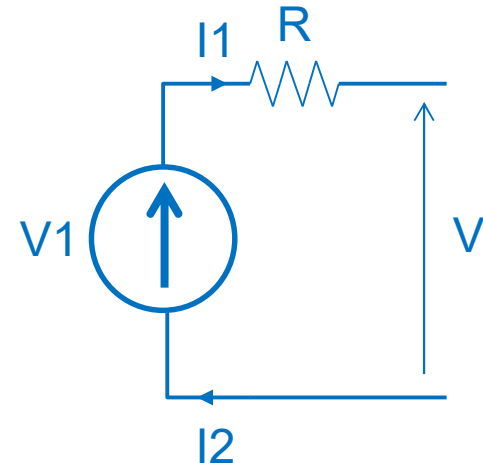


6. Current source (Norton's model)

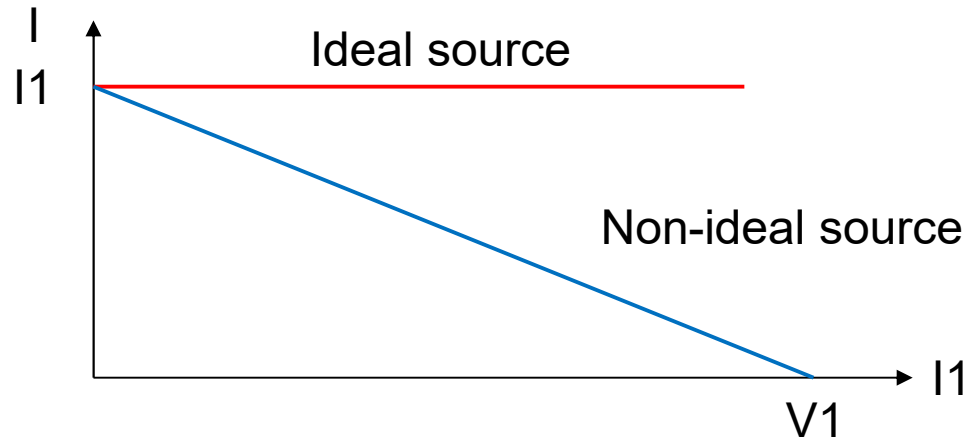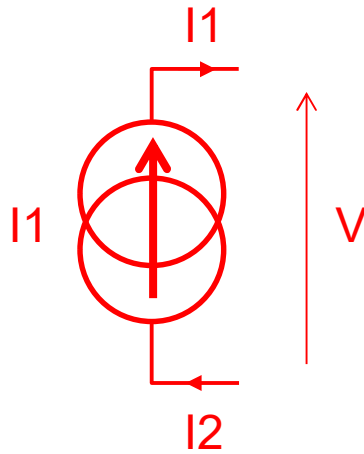


➤ Current source:

- $I_1 = |I_2|$
- voltage may be positive, negative or zero
- V_1 : open-circuit voltage
- I_1 : short-circuit current
- R : internal resistance (linear model)

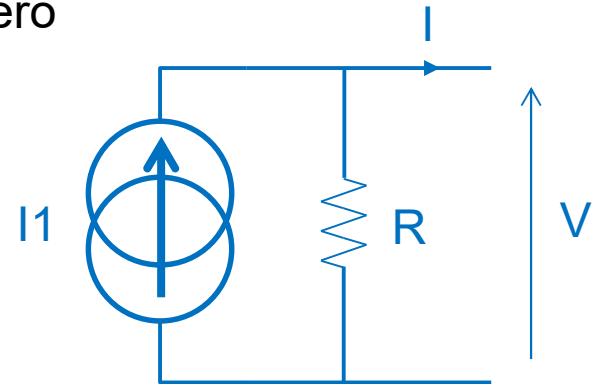

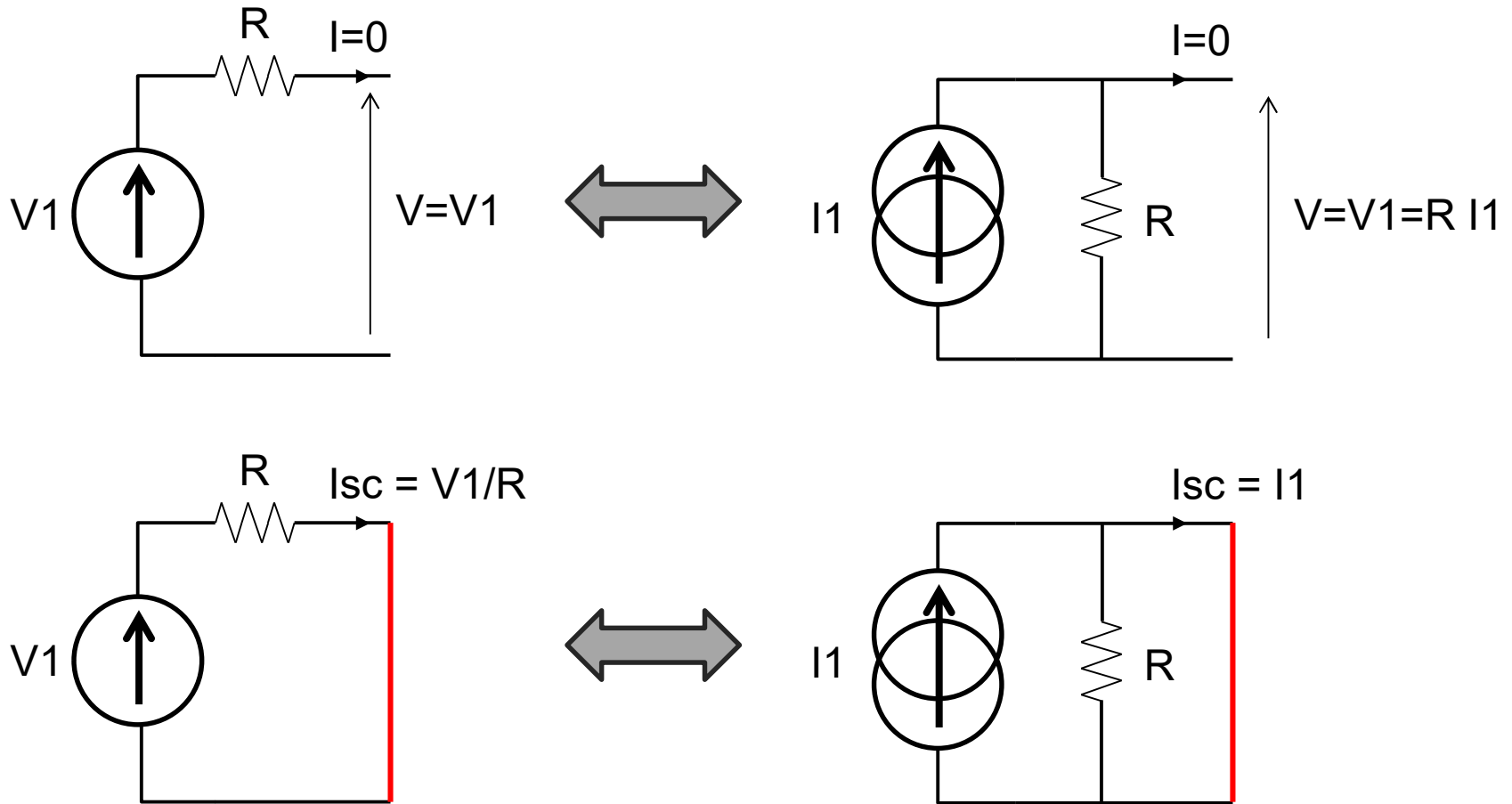7. Thevenin-Norton equivalence


- Thevenin's and Norton's models are equivalent for a **non-ideal** source



1. 8. Controlled sources


➤ Voltage/current source which value depends on another voltage/current

➤ Four possible combinations:

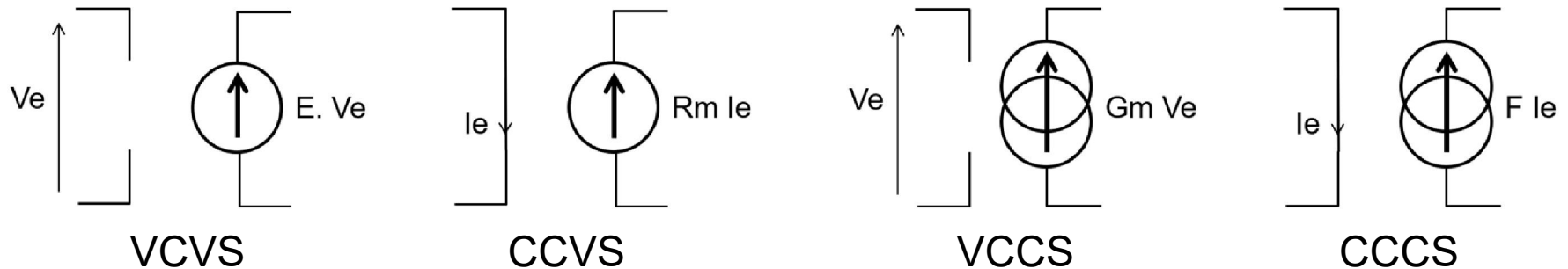

➤ Used to model complex circuits (operational amplifiers...)


➤ Unilateral devices

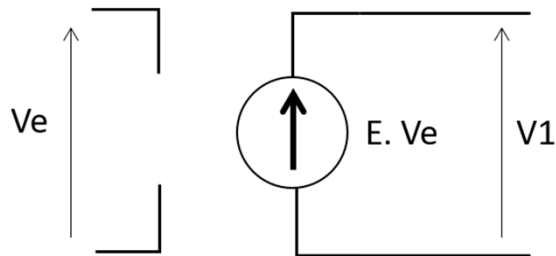

$V_1 = E V_e$ means that output voltage V_1 depends on the voltage V_e applied to the input.

$V_e = V_1 / E$ is mathematically correct. However, applying a voltage to output V_1 will **not** change the value of input voltage V_e .

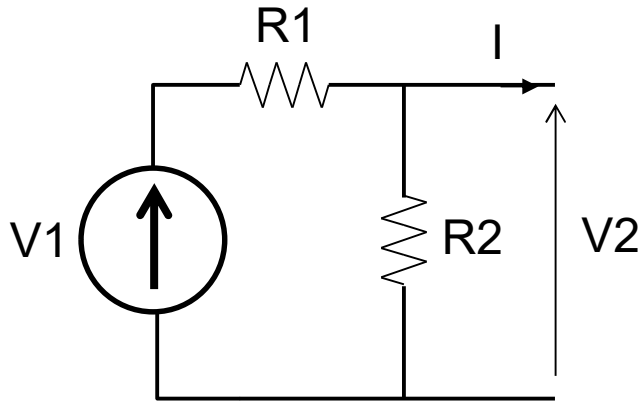
9. The voltage divider & the current divider



if $I = 0$ (Exact solution)

$$V_2 = V_1 \frac{R_2}{R_1 + R_2}$$

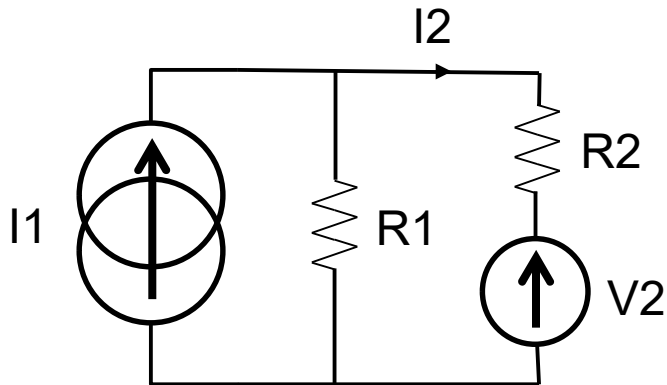Good approximation provided $I \ll \frac{V_1}{R_1}$





if $V_2 = 0$ (Exact solution)

$$I_2 = I_1 \frac{R_1}{R_1 + R_2}$$


Good approximation provided $I_1 \gg \frac{V_2}{R_1}$

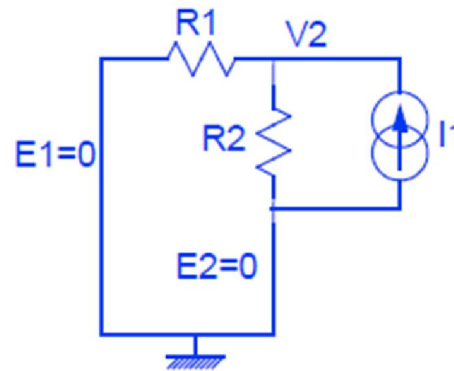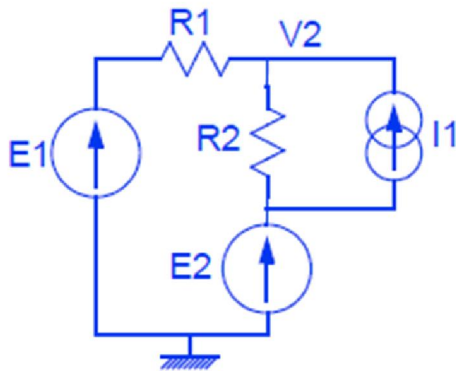10. Superimposition


- Voltage and current sources must be independent,
- Voltages and currents in the circuit are the sum of individual contributions from the sources,
- The individual contribution of source S_x is calculated when all sources but S_x are set to zero



$$V_{2a} = (R_1 // R_2) I_1$$

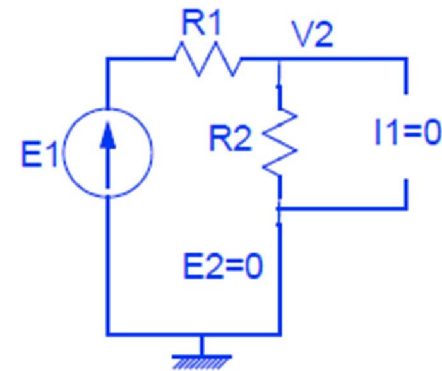

$$V_{2b} = E_1 R_2 / (R_1 + R_2)$$

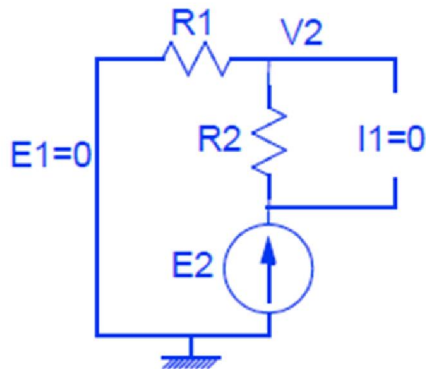


$$V_{2c} = E_2 R_1 / (R_1 + R_2)$$

$$V_2 = V_{2a} + V_{2b} + V_{2c}$$


11. The concept of equivalent impedance

- Used to model part of a complex circuit

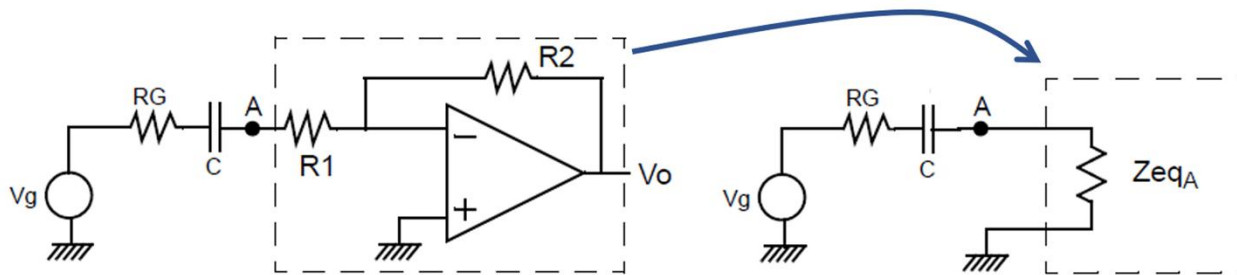Example: determine the capacitor value for a given cut-off frequency



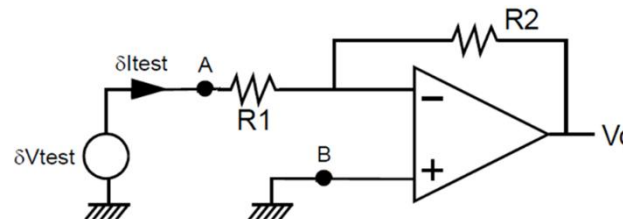- Defined as $Z_{eq} = \frac{\partial V}{\partial I}$



- May be real or complex:
 - Impedance: $Z = R + jX$
 - Admittance: $Y = G + jS$
- Linearization of the I-V characteristic at the operating point V1-I1

